

# UPDAAN

2025

## ELECTRICITY

**PHYSICS**

Lecture no - 09

**By - ER. RAKSHAK SIR**



# Topics to be covered



1

NCERT Discussion (Part-2)







How is a voltmeter connected in the circuit to measure the potential difference between two points?



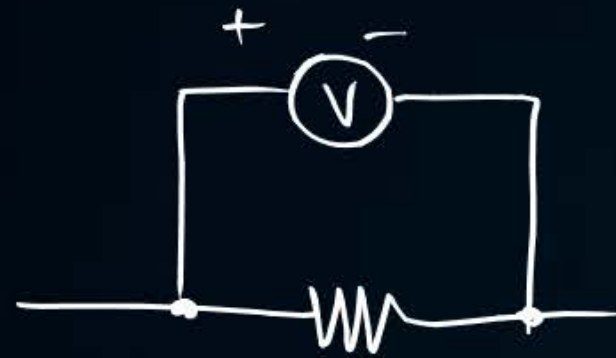Parallel  
across  
the  
two points  
on either  
side of the  
device



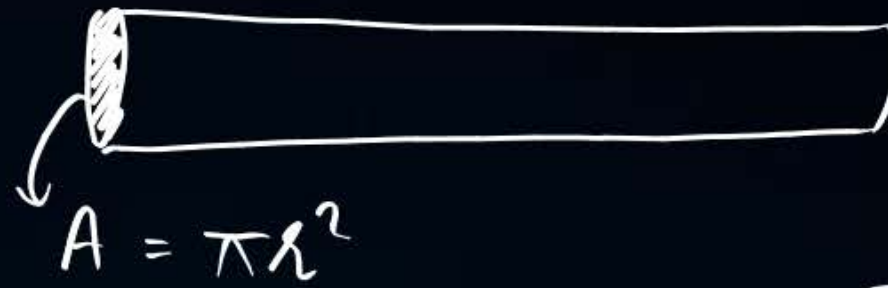

A copper wire has diameter 0.5 mm and resistivity of  $1.6 \times 10^{-8} \Omega \text{ m}$ . What will be the length of this wire to make its resistance  $10 \Omega$ ? How much does the resistance change if the diameter is doubled?

$$A = \pi r^2 \quad d = 0.5 \text{ mm} = \frac{0.5}{1000} \text{ m}$$

$$= 3.14 \times \frac{0.5}{2} \times 10^{-3} \text{ m}$$

$$\rho = 1.6 \times 10^{-8} \Omega \text{ m}$$

$$R = 10 \Omega$$

$$l = ?$$

$$R = \frac{\rho l}{A}$$

$$10 = \frac{1.6 \times 10^{-8} \times l}{3.14 \times \frac{0.5}{2} \times \frac{0.5}{2} \times 10^{-6}}$$

$$l = \frac{10 \times 3.14 \times \frac{0.5}{2} \times \frac{0.5}{2} \times 10^{-6}}{1.6 \times 10^{-8}}$$

$$l = \boxed{\phantom{0000}} \text{ m}$$

$$d \rightarrow 2d$$

$$r \rightarrow 2r$$

$$A \rightarrow$$


$$d = 2r$$

$$2d \propto 2r$$

$$A = \pi r^2$$

$$A \propto r^2$$

6<sup>th</sup> Maths

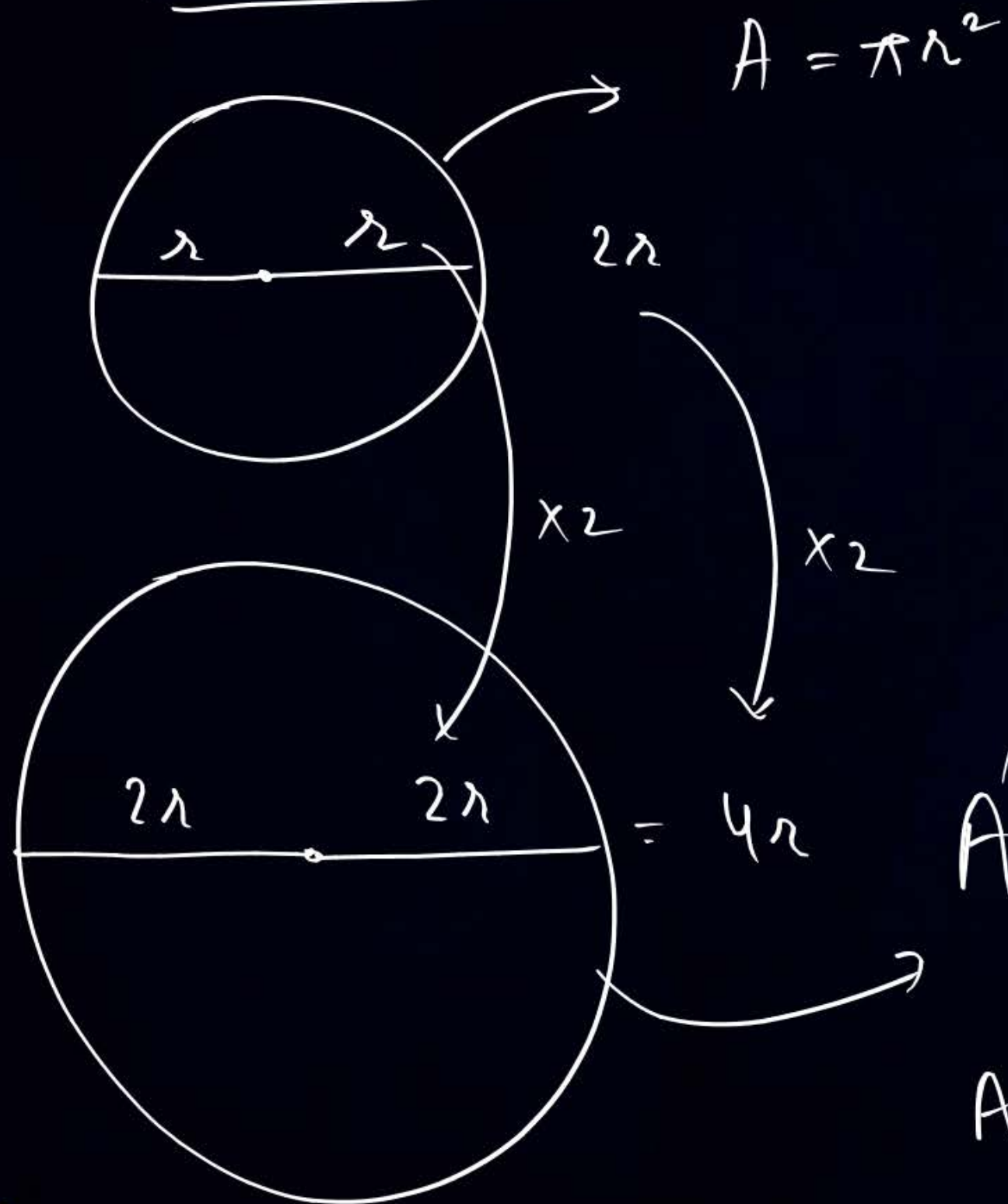

$$d \rightarrow 2d$$

$$r \rightarrow 2r$$

$$A \rightarrow 4A$$

$$R = \rho \frac{l}{A} \quad ; \quad R' = \frac{\rho l}{4A}$$

$$\frac{R'}{R} = \frac{\frac{\rho l}{4A}}{\frac{\rho l}{A}} = \frac{1}{4}$$


$$R' = \frac{R}{4}$$



The values of current  $I$  flowing in a given resistor for the corresponding values of potential difference  $V$  across the resistor are given below –

$I$ (amperes)	$I_1$ 0.5	1.0	2.0	3.0	$I_2$ 4.0
$V$ (volts)	$V_1$ 1.6	3.4	6.7	10.2	$V_2$ 13.2

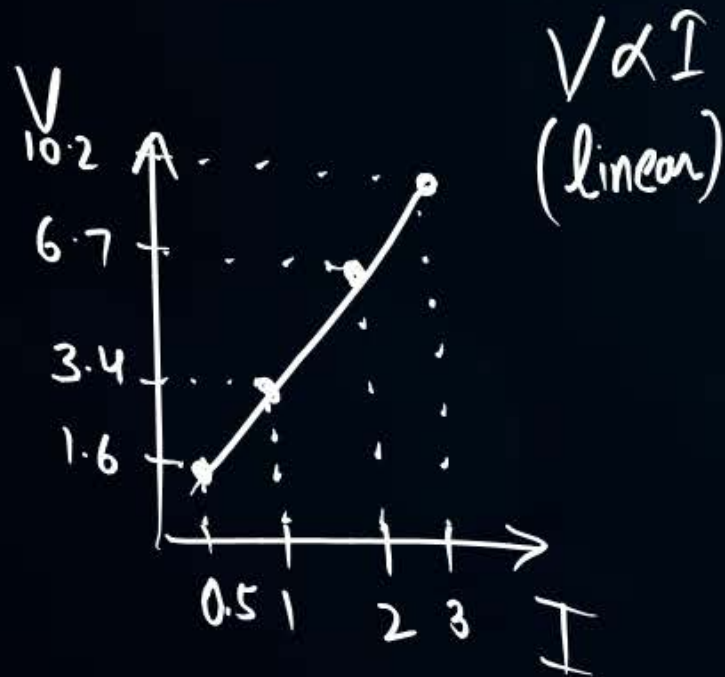Plot a graph between  $V$  and  $I$  and calculate the resistance of that resistor.



$$\text{Slope (V-I)} = \frac{\Delta V}{\Delta I} = R$$

$$= \frac{V_2 - V_1}{I_2 - I_1} = \frac{13.2 - 1.6}{4 - 0.5} = \text{--- } \Omega$$

$$R = ?$$

When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.

$$V = 12 \text{ V}$$

$$i = 2.5 \text{ mA} = 2.5 \times 10^{-3} \text{ A}$$

$$R = ?$$

$$V = iR$$


$$R = \frac{V}{i} = \frac{12}{2.5 \times 10^{-3}}$$

$$= \frac{12 \times 10^3 \times 10}{2.5}$$

$$= \frac{12 \times 100 \times 10^2}{2.5}$$

$$= 4800 \, \Omega$$

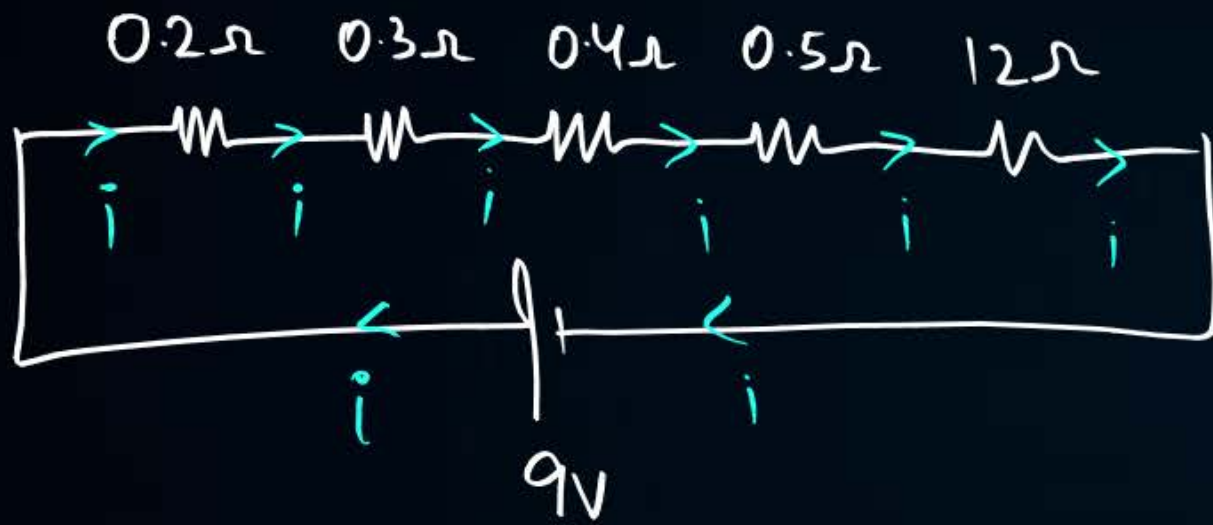A battery of 9 V is connected in series with resistors of  $0.2\ \Omega$ ,  $0.3\ \Omega$ ,  $0.4\ \Omega$ ,  $0.5\ \Omega$  and  $12\ \Omega$ , respectively. How much current would flow through the  $12\ \Omega$  resistor?



$$R_t = R_1 + R_2 + R_3 + \dots$$

$$R_t = 0.2 + 0.3 + 0.4 + 0.5 + 12$$


$$R_t = 13.4\ \Omega$$

$$V = iR$$

$$i = \frac{V}{R} = \frac{9}{13.4}\text{ A}$$



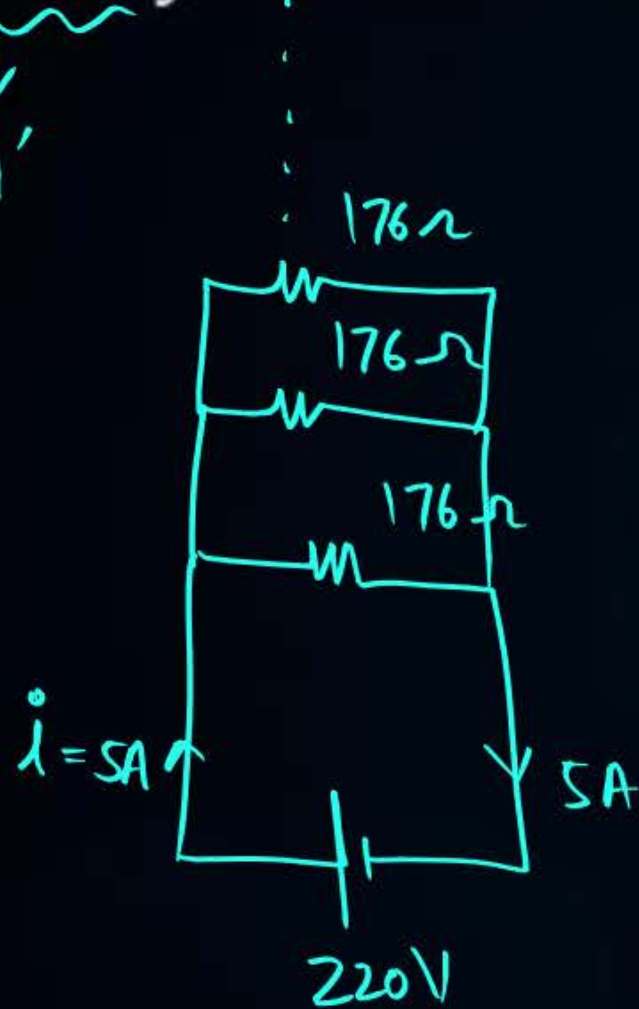How many  $176\ \Omega$  resistors (in parallel) are required to carry 5 A on a 220 V line?



$$V_t = 220\text{ V}$$

$$i_t = 5\text{ A}$$

$$R_t = ?$$

$$V = iR$$

$$220 = 5 \times R_p$$

$$R_p = 44\ \Omega$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


$$\frac{1}{44} = \frac{1}{176} + \frac{1}{176} + \frac{1}{176} + \dots \quad n \text{ times}$$

$$\frac{1}{44} = \frac{n}{176}$$

$$\frac{176}{44} = n$$


$$n = 4$$

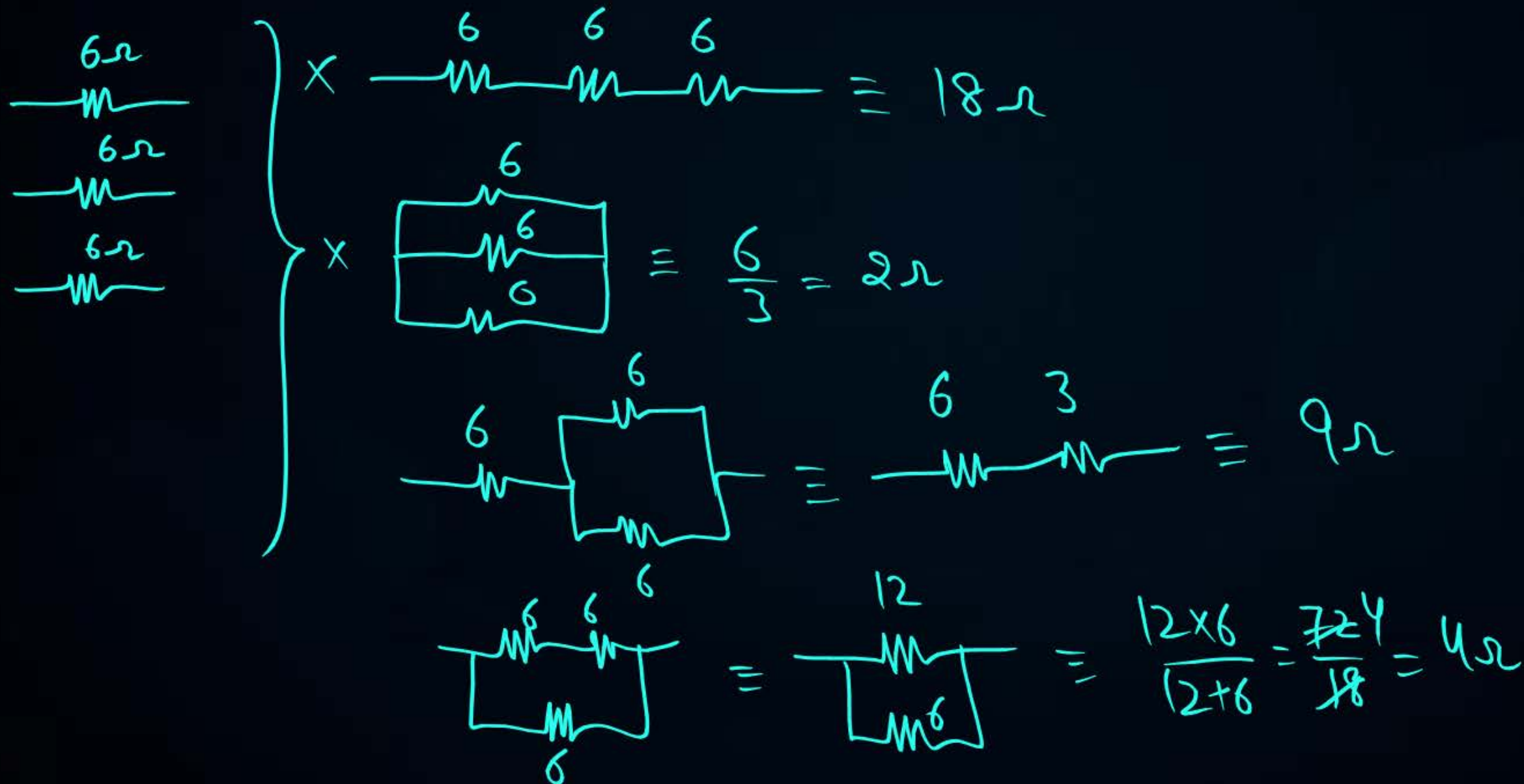Show how you would connect three resistors, each of resistance  $6\ \Omega$ , so that the combination has a resistance of (i)  $9\ \Omega$ , (ii)  $4\ \Omega$ .





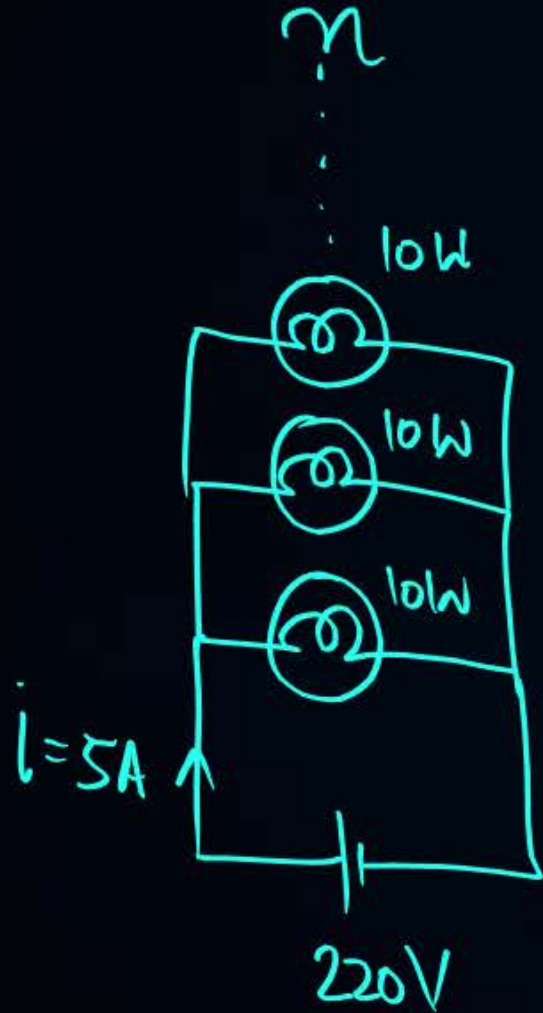Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel with each other across the two wires of 220 V line if the maximum allowable current is 5 A?



$$\begin{aligned}
 P_t &= V \times I \\
 &= 220 \times 5 \\
 &= 1100 \text{ W}
 \end{aligned}$$

$$P_{\text{total}} = P_1 + P_2 + P_3 + P_4 + \dots + n$$

$$1100 = 10 + 10 + 10 + 10 + \dots + n$$

$$1100 = 10n$$

$$n = 110 \text{ Bulbs}$$

A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of  $24\ \Omega$  resistance, which may be used separately, in series, or in parallel. What are the currents in the three cases?


Separate



$$V = iR$$

$$i_1 = \frac{V}{R} = \frac{220}{24}\text{ A}$$


Series

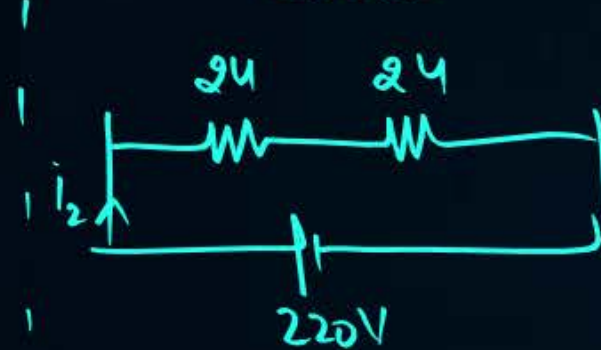

$$V = iR_s$$

$$i_2 = \frac{V}{R_s} = \frac{220}{48}\text{ A}$$

Parallel

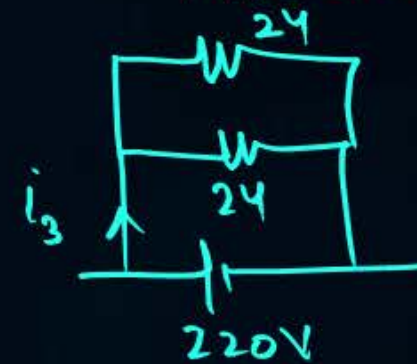


$$V = i_3 R_p$$

$$i_3 = \frac{V}{R_p} = \frac{220}{12}\text{ A}$$



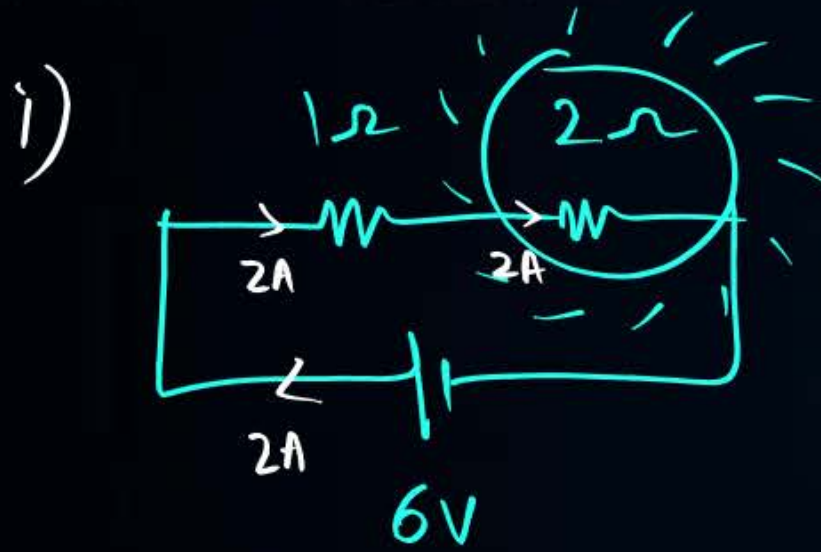Compare the power used in the  $2\ \Omega$  resistor in each of the following circuits: (i) a  $6\ \text{V}$  battery in series with  $1\ \Omega$  and  $2\ \Omega$  resistors, and (ii) a  $4\ \text{V}$  battery in parallel with  $12\ \Omega$  and  $2\ \Omega$  resistors.



$$R_t = 3\ \Omega$$

$$V = 6\ \text{V}$$

$$i = \frac{V}{R} = \frac{6}{3} = 2\ \text{A}$$


$$i = 2\ \text{A}$$

$$\begin{aligned} P &= i^2 R \\ &= 2^2 \times 2 \\ P &= 8\ \text{W} \end{aligned}$$



$$P = \frac{V^2}{R} = \frac{(4)^2}{2} = \frac{16}{2} = 8\ \text{W}$$

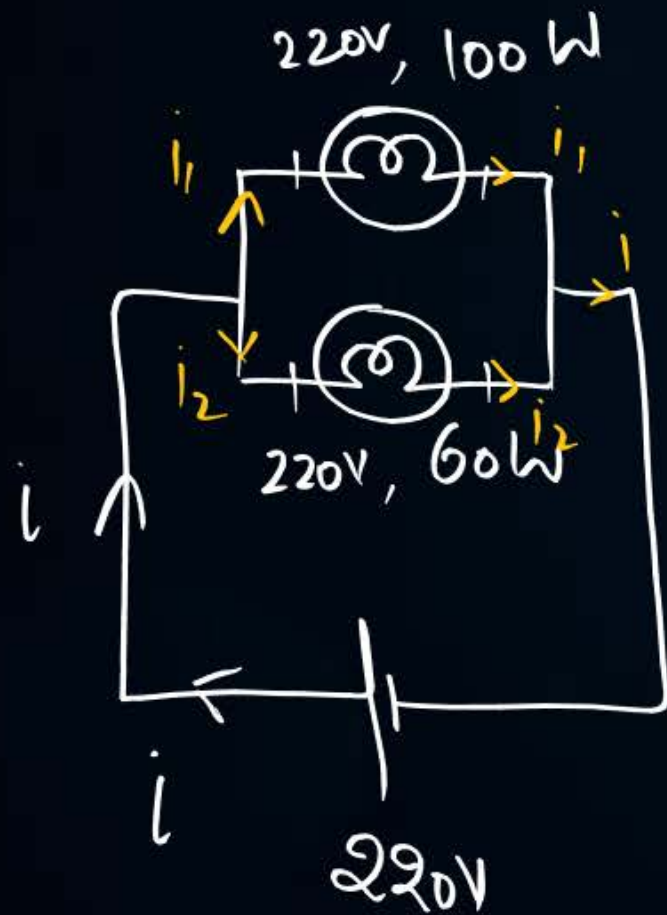Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V?



M-1

$$\begin{aligned}
 P_{\text{total}} &= P_1 + P_2 \\
 &= 100 + 60 \\
 &= 160 \text{ W}
 \end{aligned}$$

$$\begin{aligned}
 P &= V \times i \\
 160 &= 220 \times i
 \end{aligned}$$

$$i = \frac{160}{220} \text{ A}$$

M-2

$$\begin{aligned}
 P &= Vi \\
 60 &= 220 \times i_2 \\
 \frac{60}{220} \text{ A} &= i_2
 \end{aligned}$$

$$\begin{aligned}
 P &= Vi \\
 100 &= 220 \times i_1 \\
 \frac{100}{220} \text{ A} &= i_1
 \end{aligned}$$

$$\begin{aligned}
 i &= i_1 + i_2 \\
 &= \frac{60}{220} + \frac{100}{220} \\
 i &= \frac{160}{220} \text{ A}
 \end{aligned}$$



Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes?

TV

$$P = 250 \text{ W} = \frac{250}{1000} \text{ kW}$$

$$t = 1 \text{ h}$$

$$E = P \times t$$

$$= \frac{250}{1000} \times 1$$

$$= 0.25 \text{ kWh}$$

Toaster

$$P = 1200 \text{ W} = \frac{1200}{1000} \text{ kW}$$

$$t = 10 \text{ min} = \frac{10}{60} \text{ h}$$

$$E = P \times t$$

$$= \frac{1200}{1000} \times \frac{10}{60}$$

$$= \frac{12}{60} = 0.2 \text{ kWh}$$

TV > Toaster



An electric heater of resistance 8 ~~W~~ draws 15 A from the service mains 2 hours. Calculate the rate at which heat is developed in the heater.

~~X 60~~  
X 60

$$\begin{aligned}\text{Power} &= I^2 R \\ &= (15)^2 \times 8 \\ &= 15 \times 15 \times 8 \text{ Watt}\end{aligned}$$



Explain the following.

- (a) Why is the tungsten used almost exclusively for filament of electric lamps?
- (b) Why are the conductors of electric heating devices, such as bread-toasters and electric irons, made of an alloy rather than a pure metal?
- (c) Why is the series arrangement not used for domestic circuits?
- (d) How does the resistance of a wire vary with its area of cross-section?
- (e) Why are copper and aluminium wires usually employed for electricity transmission?

① Cheap  
② Light

Good Conductor

MP  $\uparrow$   $\rightarrow$   $3380^{\circ}\text{C}$   $\rightarrow$  heat retain  $\rightarrow$  glow  
R  $\uparrow$

Notes  
S  $\downarrow$  R  $\downarrow$  H  $\downarrow$   $\rightarrow$  Parallel  $\checkmark$  Series  $\times$

$$R \propto \frac{1}{A}$$



THANK  
YOU

