

# UPDAAN

2025

## ELECTRICITY

PHYSICS

Lecture -06

By - ER. RAKSHAK SIR





# Topics to be covered



- 1 SERIES CIRCUIT ✓ (Part - 02)
- 2 PARALLEL CIRCUIT ✓ (Part - 02)
- 3 COMBINATION OF RESISTORS (Practive)
- 4 RESISTANCE OF AMMETER AND VOLTMETER
- 5 WORKING OF RHEOSTAT



# 5-min Revision

Series







$$R_s = R_1 + R_2 + R_3 \dots$$

Parallel


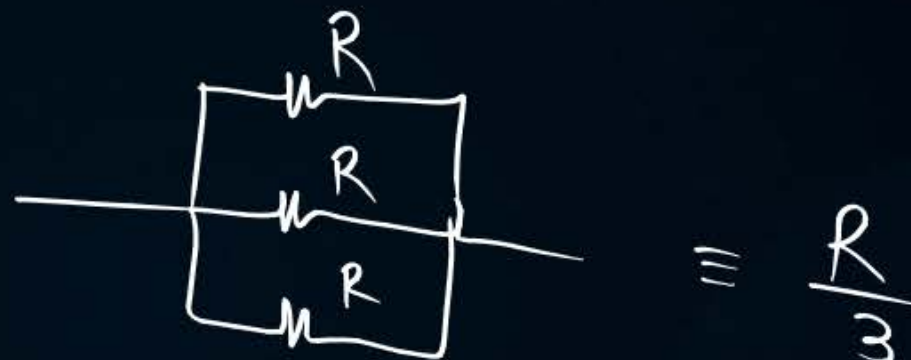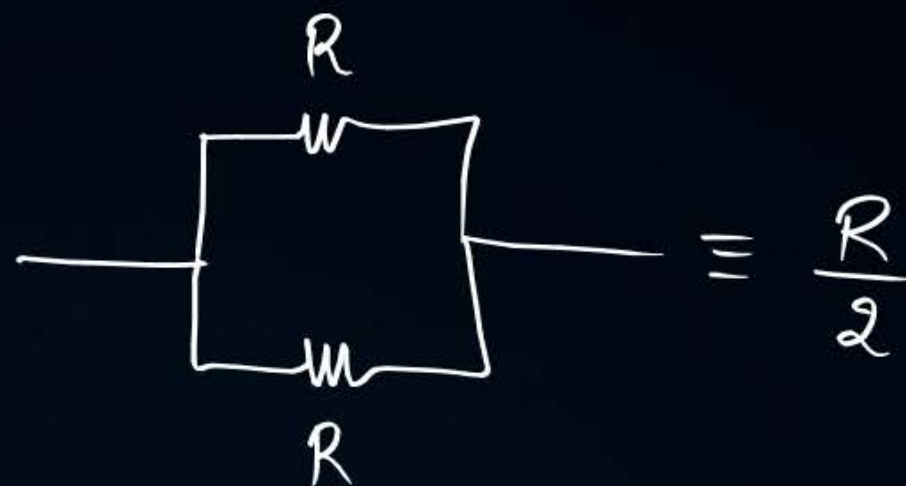
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$



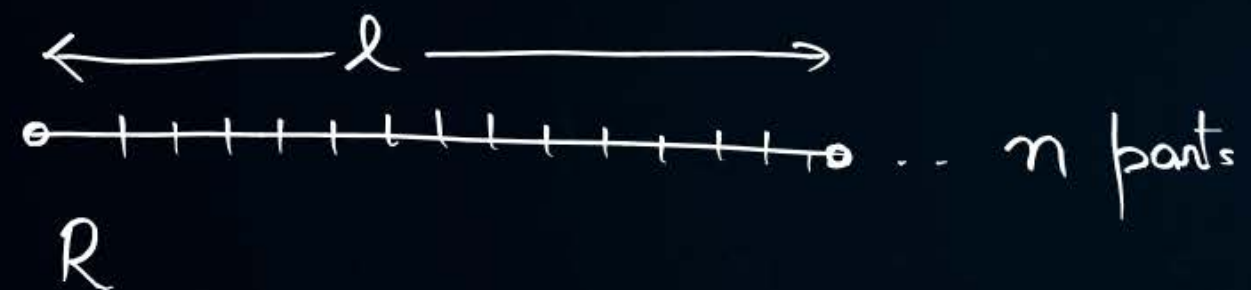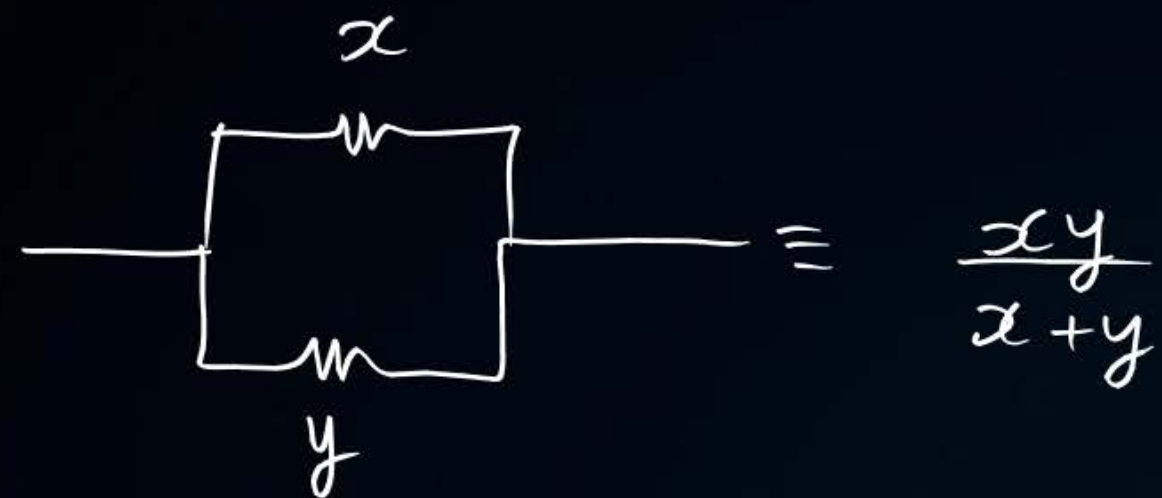

$n$ -parts  
are joined  
in parallel  $\rightarrow R'$

$$\frac{R}{R'} = \frac{n^2}{1}$$




# QUESTION

H.W.




A piece of wire of resistance  $R$  is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is  $R'$ , then the ratio  $(R/R')$  is:

$R$

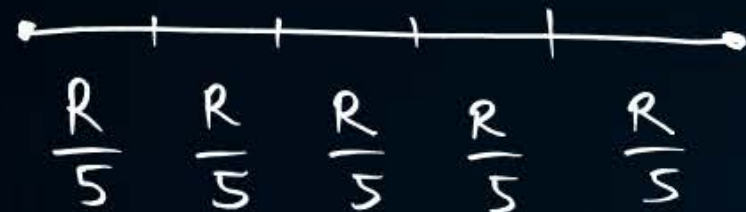

$$\frac{1}{R'} = \frac{25}{R}$$

$$\frac{R}{R'} = 25$$

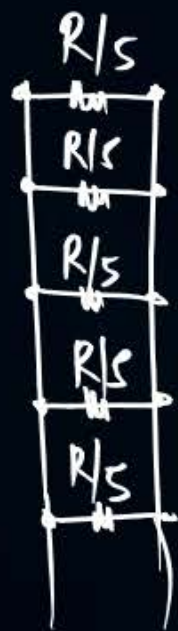

$$\frac{1}{R'} = \frac{1}{R/5} + \frac{1}{R/5} + \frac{1}{R/5} + \frac{1}{R/5} + \frac{1}{R/5}$$

$$\frac{1}{R'} = \frac{5}{R} + \frac{5}{R} + \frac{5}{R} + \frac{5}{R} + \frac{5}{R} = \frac{25}{R}$$

**A** 1/25

**B** 1/5


**C** 5

**D** 25

# QUESTION

H.W.

Shortcut

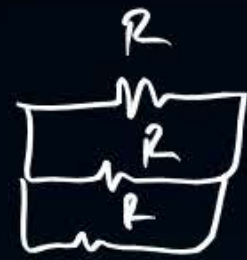


$$\left( \frac{R}{n} \right) = 44 \Rightarrow \frac{176}{n} = 44 \Rightarrow n = 4$$



How many 176 Ω resistors (in parallel) are required to carry 5 A on a 220 V line?


number 'n' = ?

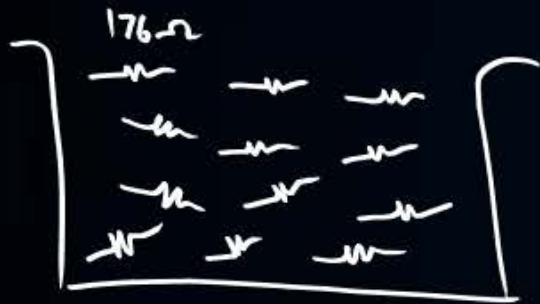

$$V = 220V$$

$$I = 5A$$
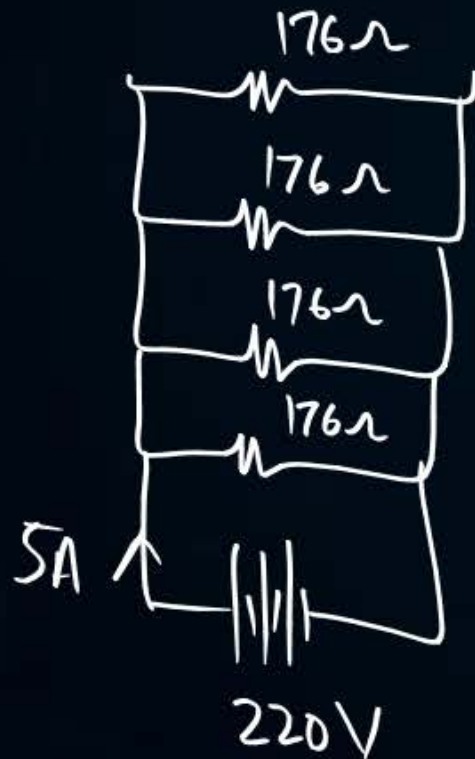
$$R_t = \frac{V}{I} = \frac{220}{5} = 44\Omega$$



$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



$$\frac{1}{44} = \frac{1}{176} + \frac{1}{176} + \frac{1}{176} + \dots + n \text{ terms}$$

$$\frac{1}{44} = n \times \frac{1}{176}$$

$$\frac{176}{44} = n$$

$$n = 4$$

## PRACTICE PROBLEMS 1 :

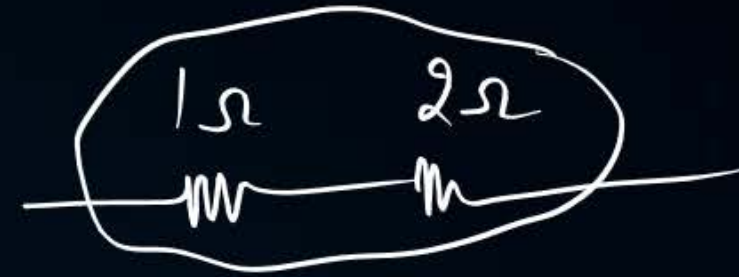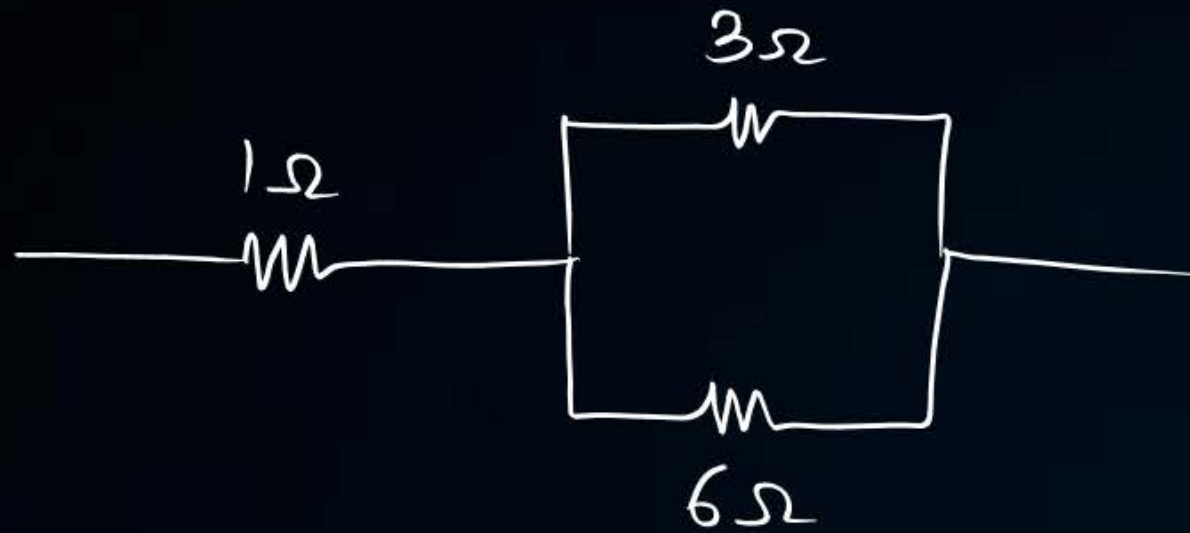


$$R_s = 1\Omega + 2\Omega = \underline{\underline{3\Omega}} \quad \underline{\underline{\text{Ans}}}$$

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3} = \frac{1+2}{6} = \frac{3}{6}$$

$$R_p = 2\Omega$$



## PRACTICE PROBLEMS 2:

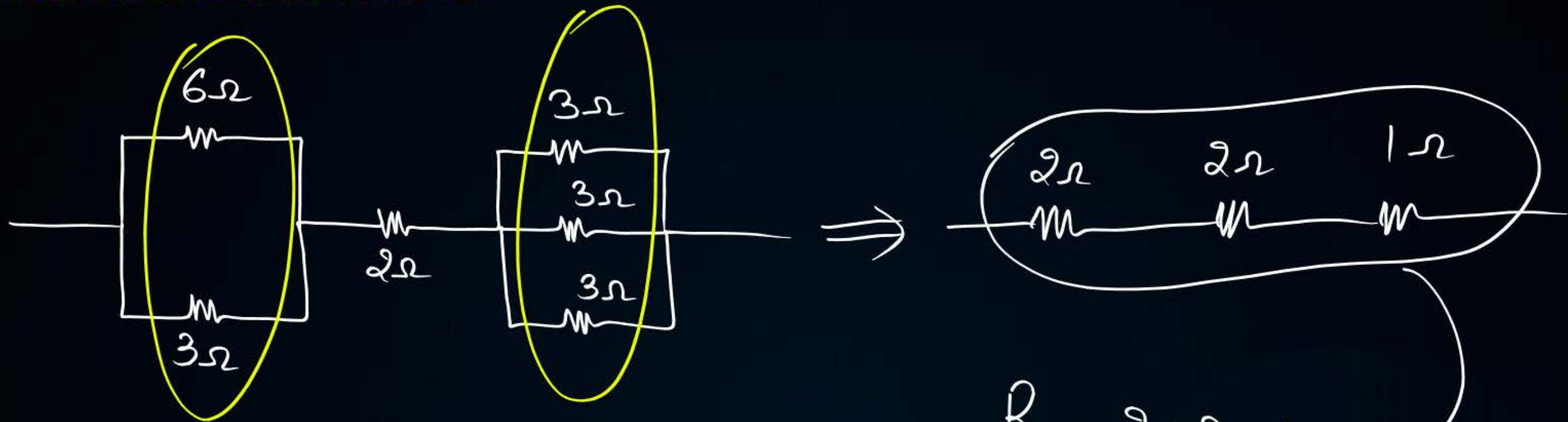

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{R_p} = \frac{1+2}{6} = \frac{3}{6}$$

$$R_p = 2\Omega$$

$$\frac{1}{R_p} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3}$$



$$\frac{1}{R_p} = \frac{3}{3}$$

$$R_p = 1\Omega$$

$$R_s = 2 + 2 + 1$$
$$= 5\Omega$$



Ex-3

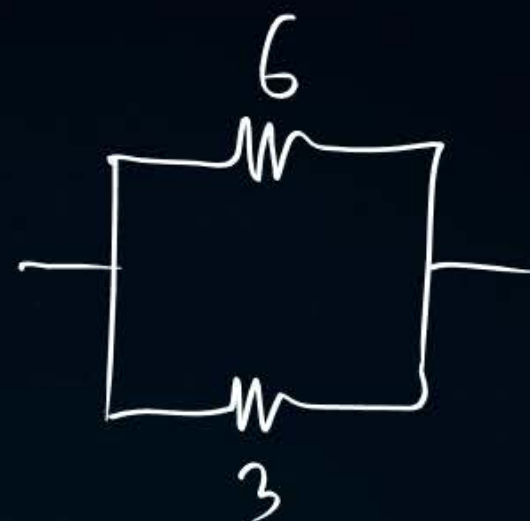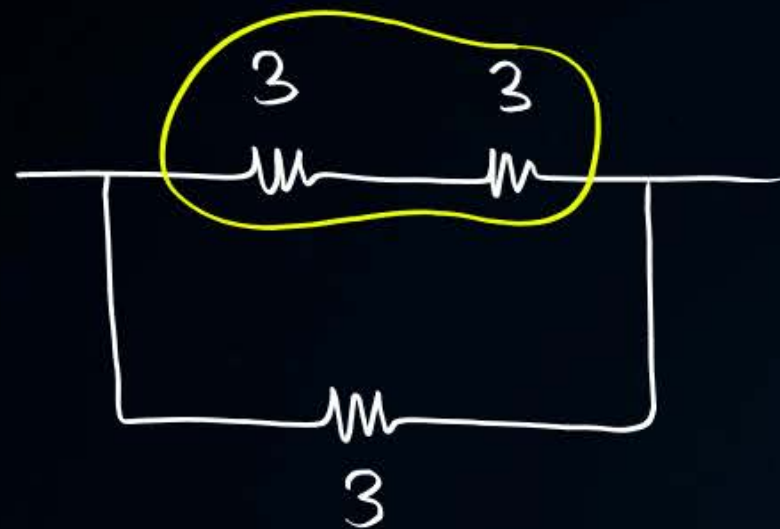

$$\begin{aligned} R_s &= R_1 + R_2 \\ &= 3 + 3 \\ &= 6\Omega \end{aligned}$$


$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{R_p} = \frac{1+2}{6} = \frac{3}{6} = \frac{1}{2}$$


$$\frac{1}{R_p} = \frac{1}{2}$$

$$\boxed{R_p = 2\Omega} \text{ Ans}$$

Ex-4

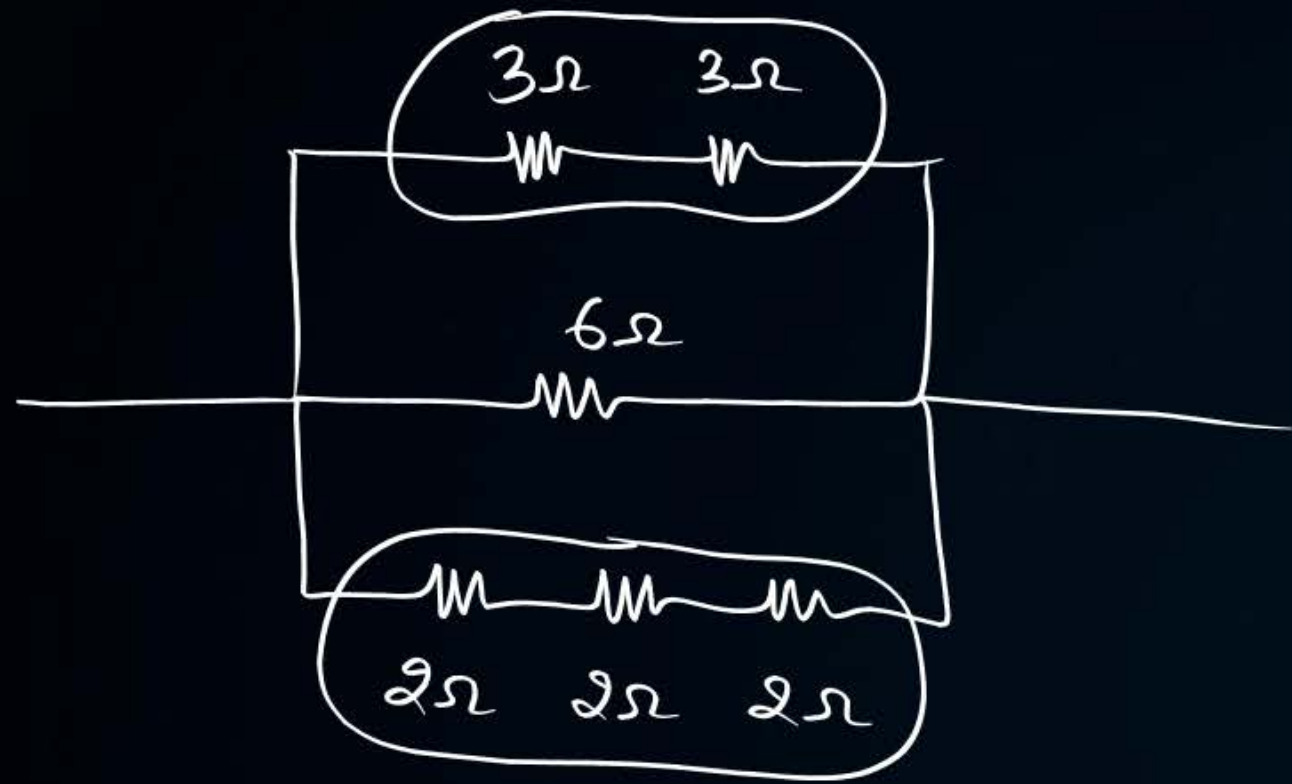

$\equiv$

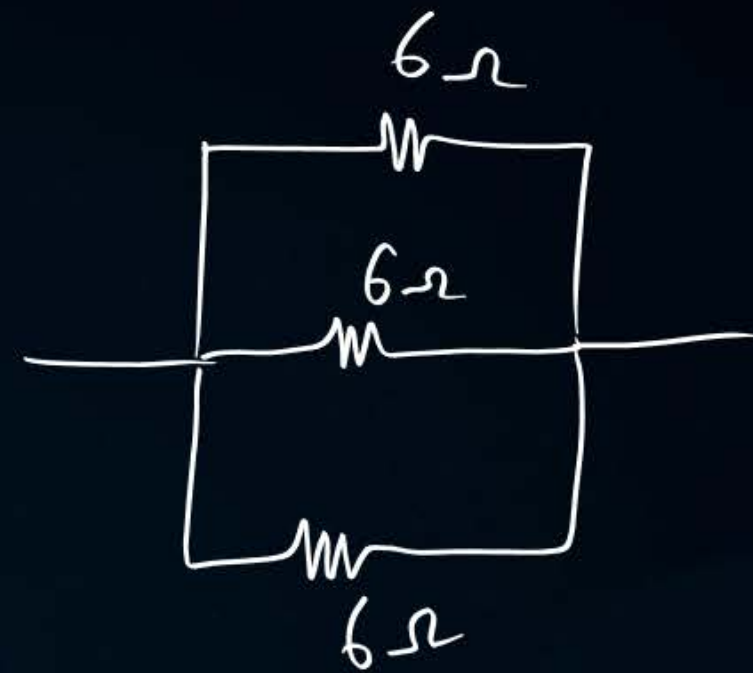


$\equiv 2\Omega$




Ex-5 find the readings in

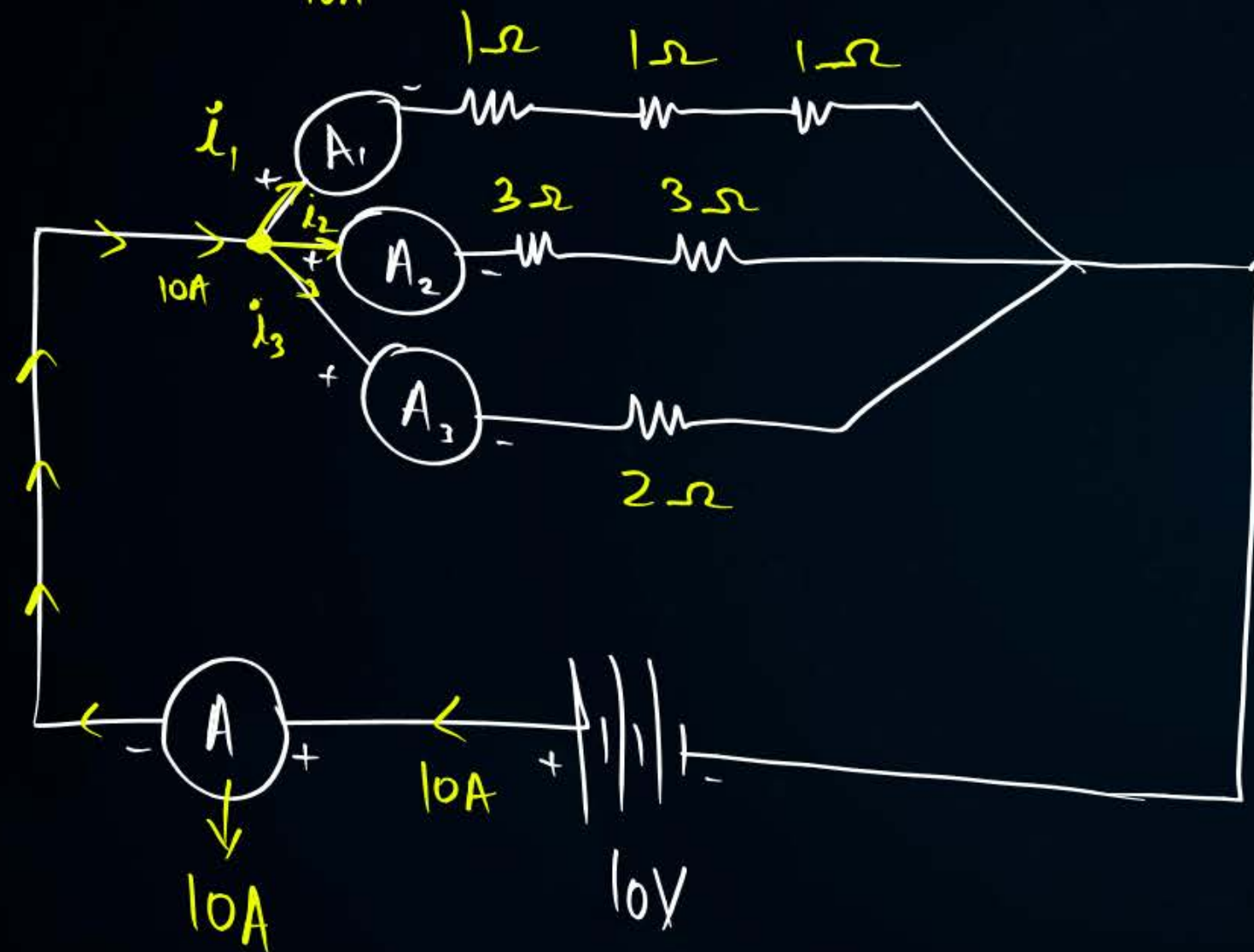$A, A_1, A_2, A_3$   
 $10A \quad 3.33A \quad 1.67A \quad 5A$








$$\frac{1}{R_p} = \frac{1}{3} + \frac{1}{6} + \frac{1}{2} = \frac{2+1+3}{6} = \frac{6}{6}$$

$$R_t = 1\Omega, V = 10V, I = \frac{V}{R} = \frac{10}{1} = 10A$$

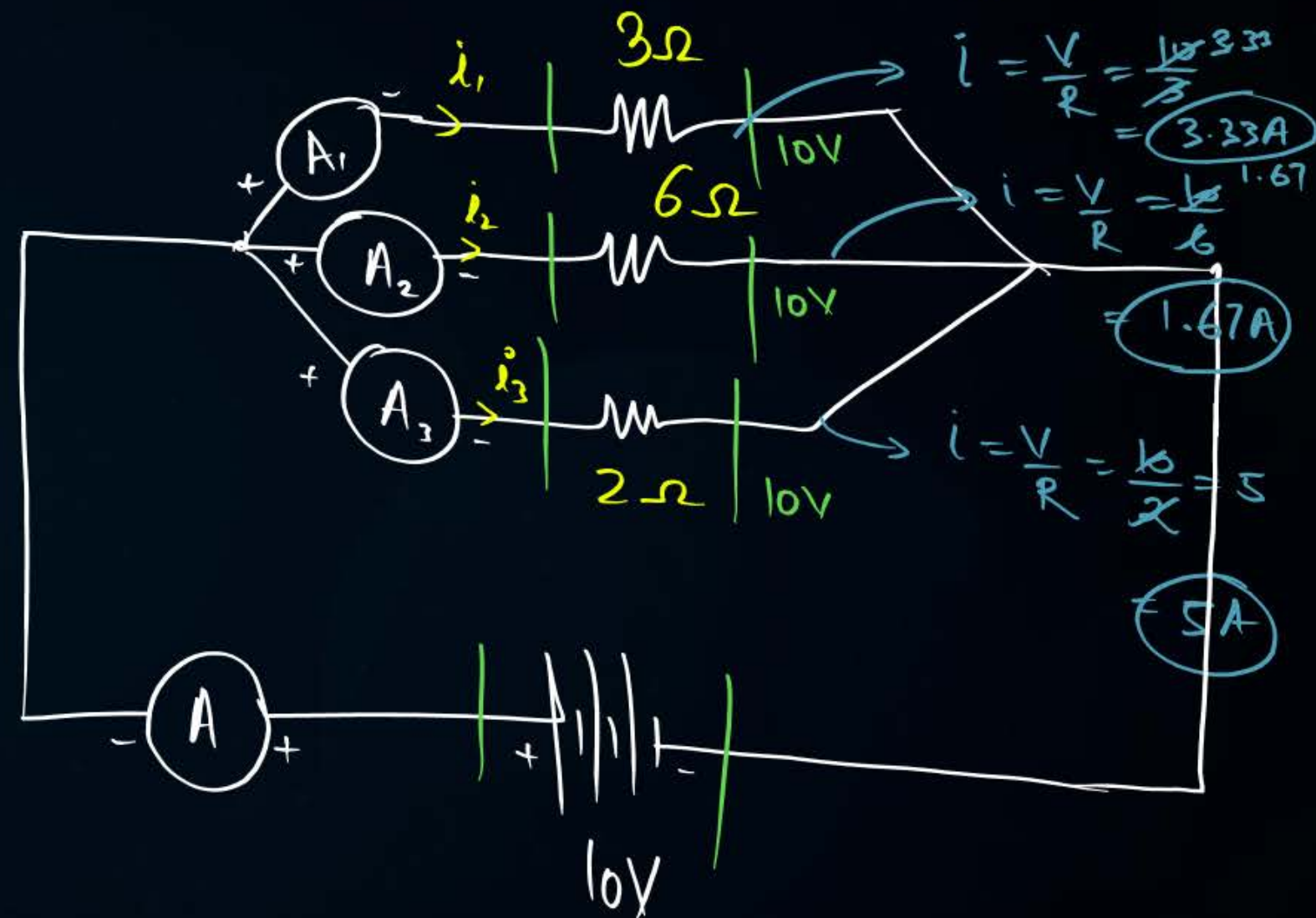




Ques 16

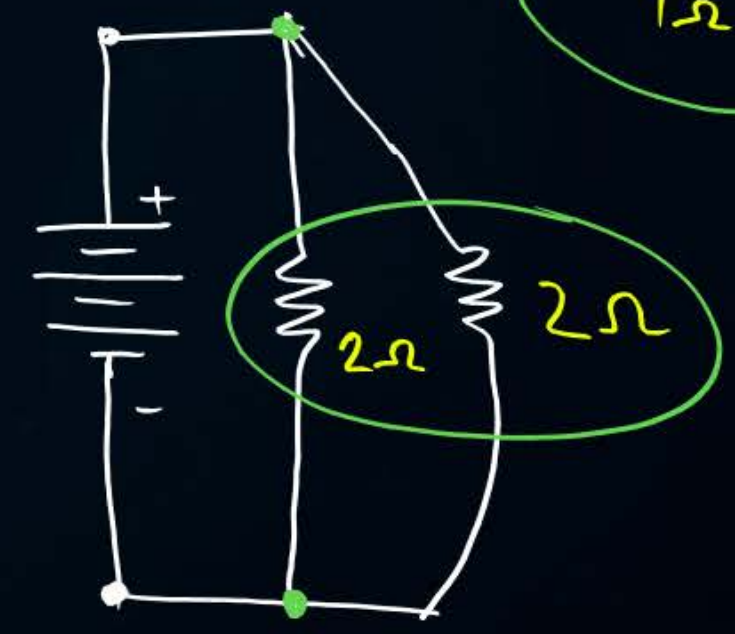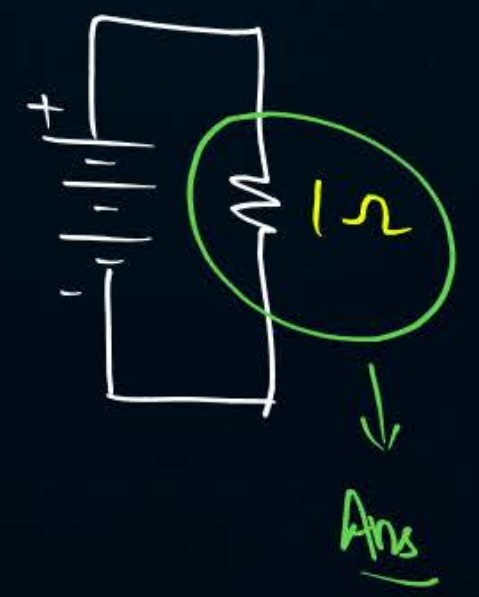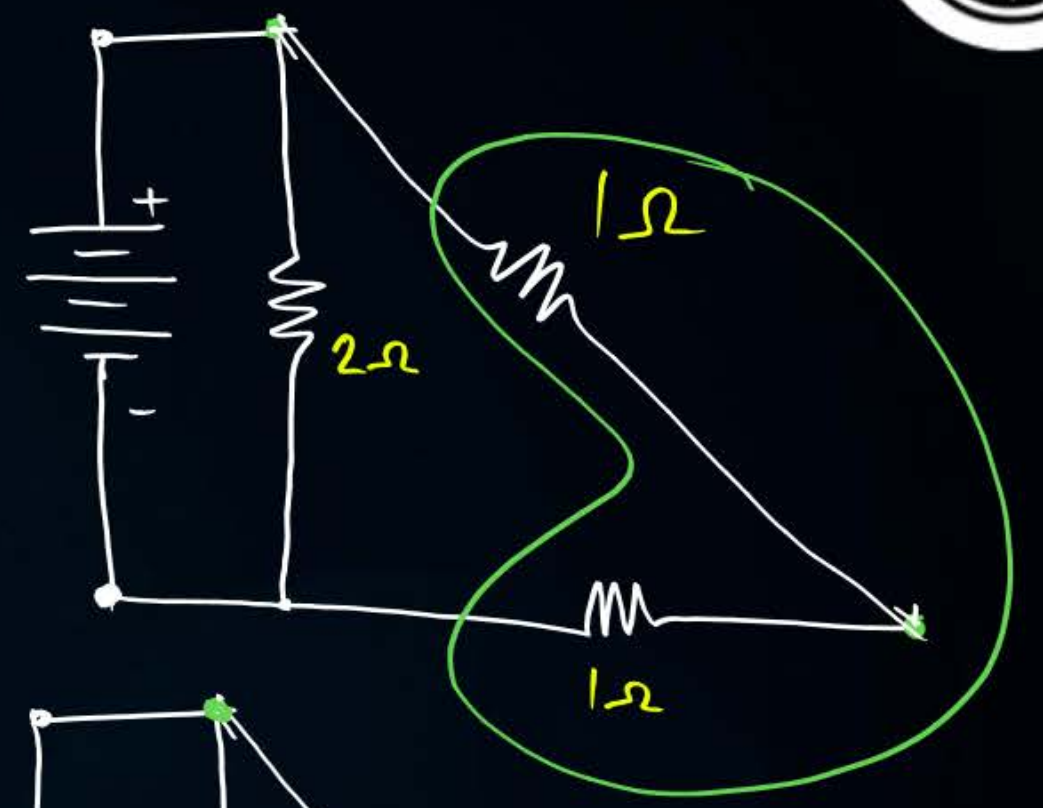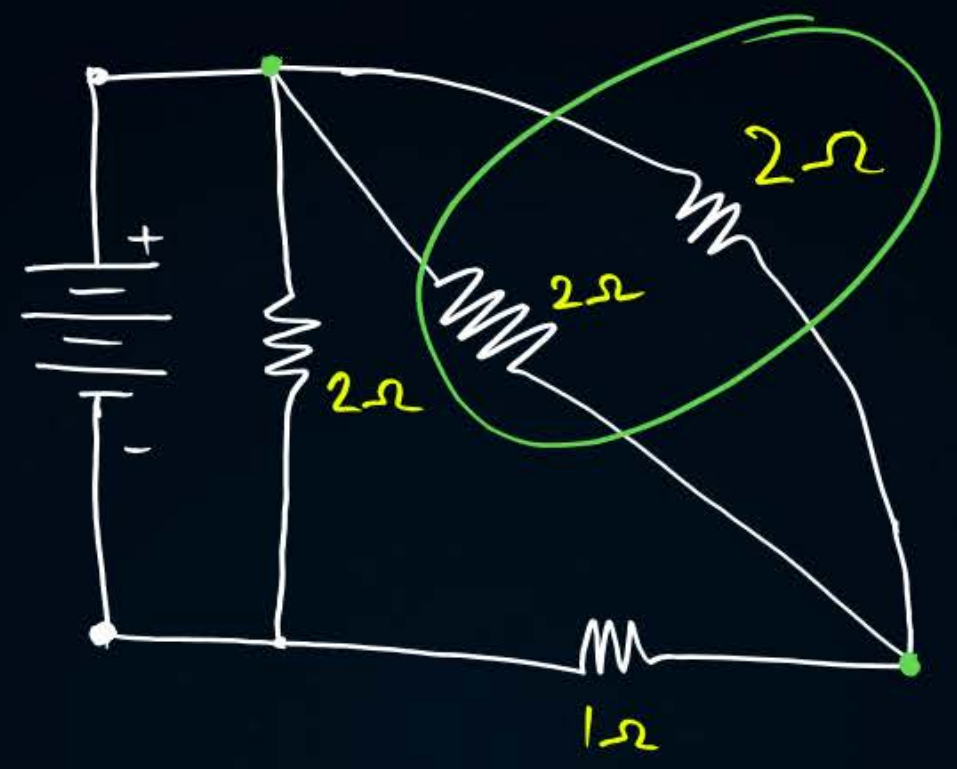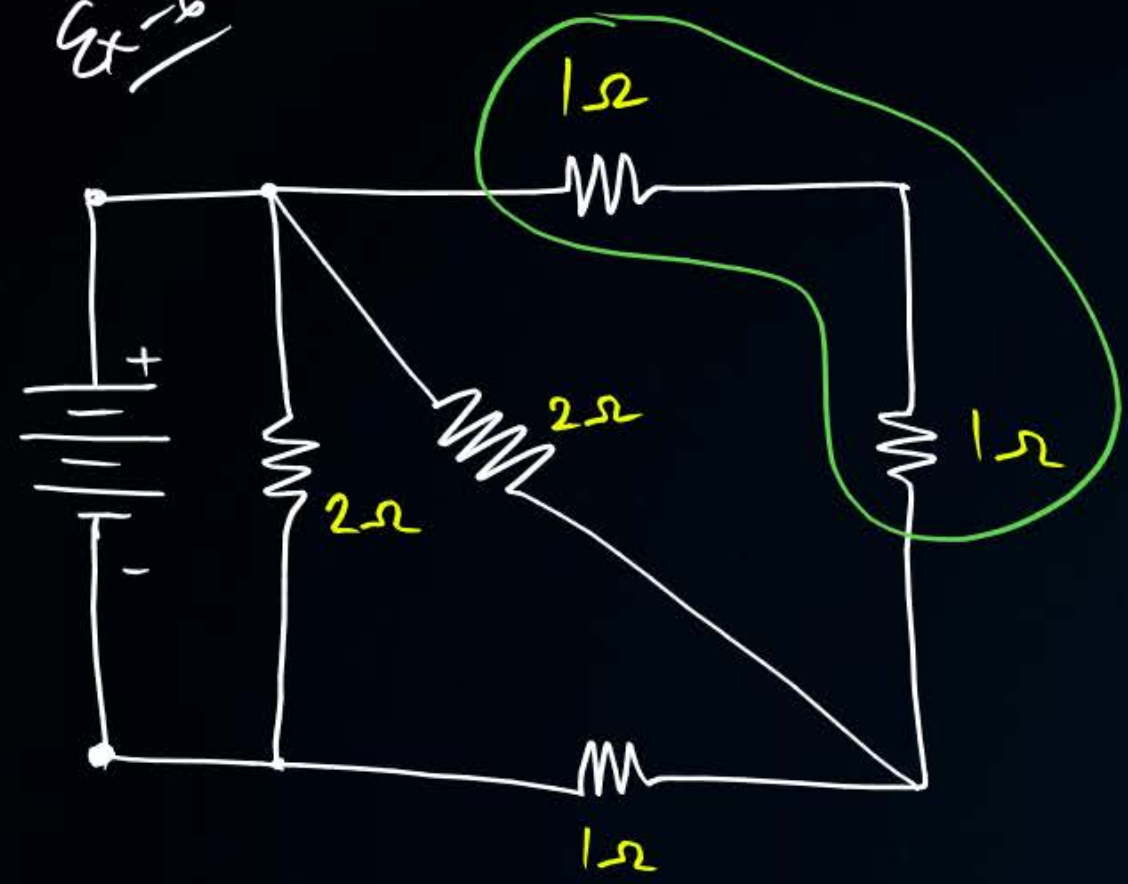

Q.1

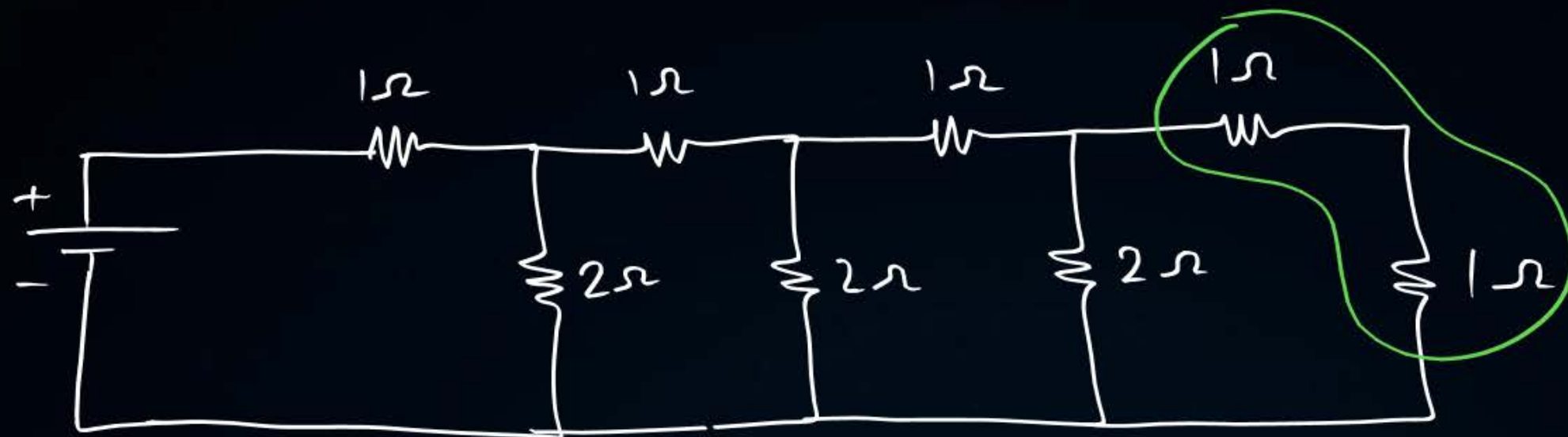

## QUESTION






How can three resistors each of resistances  $3\ \Omega$  be connected to give a total resistance of

(i)  $4.5\ \Omega$


(ii)  $2\ \Omega$

X Pure Series :-   $\equiv 9\ \Omega$

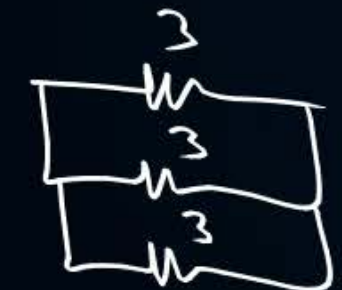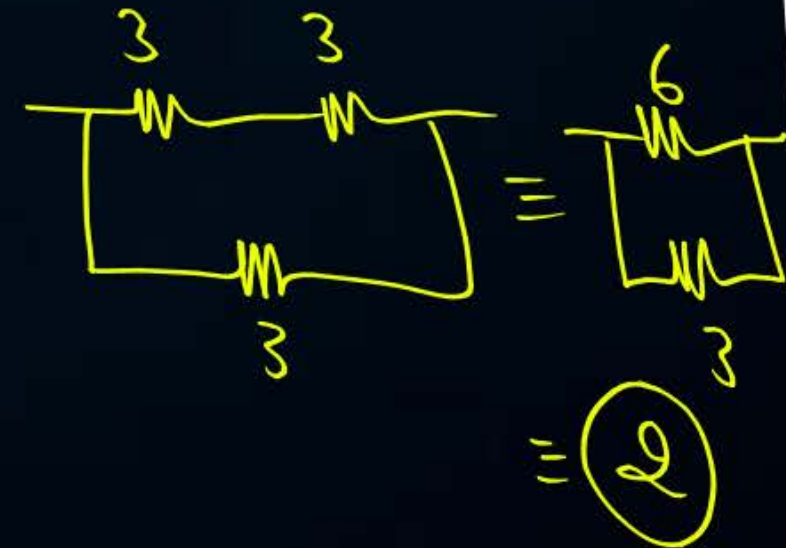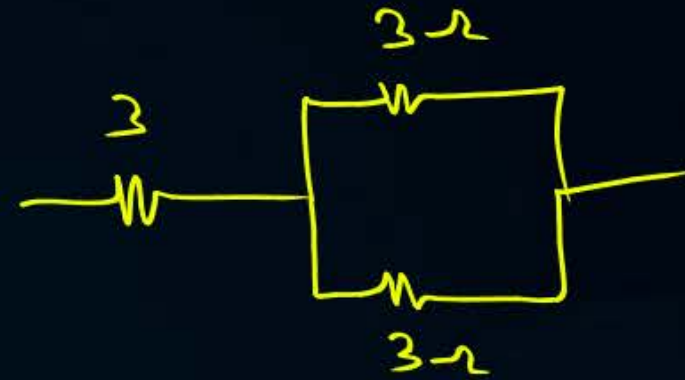X Pure Parallel :-   $\frac{1}{R_p} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3} = \frac{3}{3}$   
 $R_p = 1\ \Omega$



NOTE

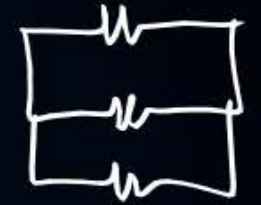



## QUESTION




Show how you would connect three resistors, each of resistance  $6\ \Omega$ , so that the combination has a resistance of

(i)  $9\ \Omega$


Pure Series —  $6 + 6 + 6 = 18\ \Omega$  ✗

Pure Parallel —  $\frac{1}{6} + \frac{1}{6} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2} \Rightarrow 2\ \Omega$  ✗

(ii)  $4\ \Omega$

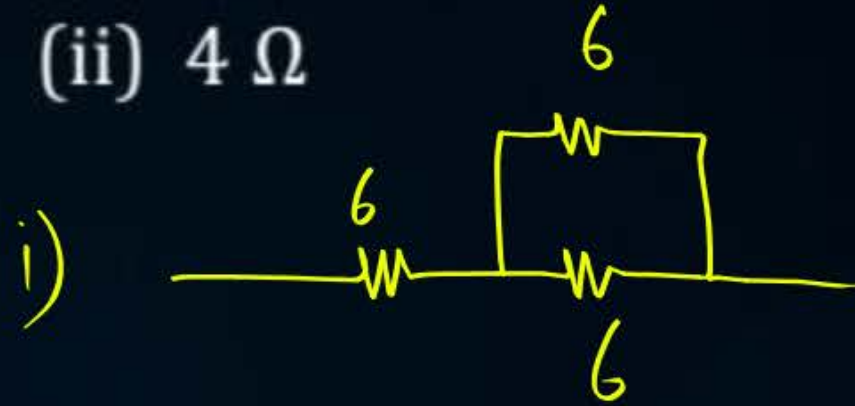

$6 + 3 = 9\ \Omega$

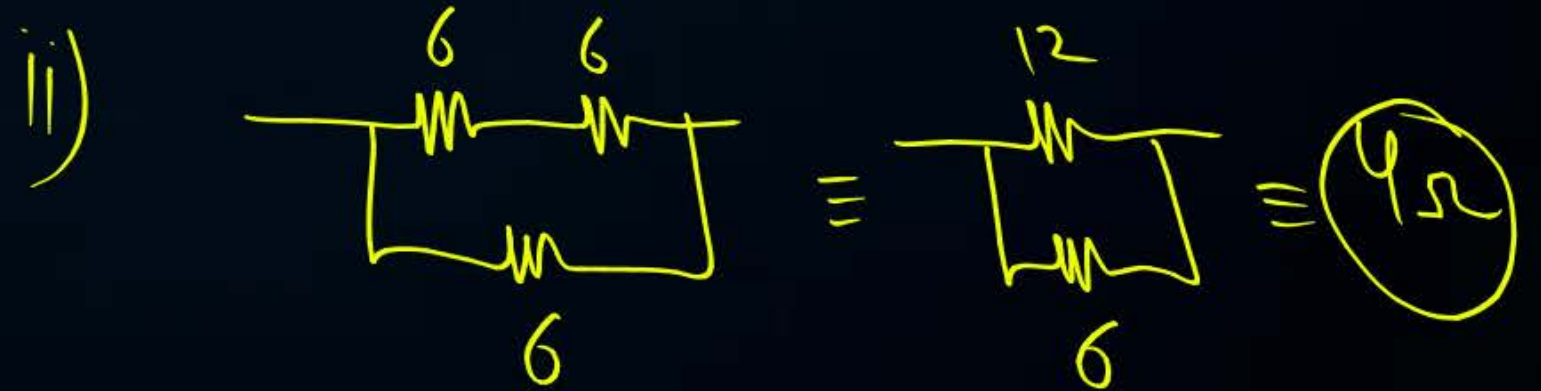

$\equiv 12 + 6 = 4\ \Omega$

## QUESTION


H.W.



If in figure,  $R_1 = 10\ \Omega$ ,  $R_2 = 40\ \Omega$ ,  $R_3 = 30\ \Omega$ ,  $R_4 = 20\ \Omega$ ,  $R_5 = 60\ \Omega$ , and a  $12\text{ V}$  battery is connected to the arrangement. Calculate:

- (a) The total resistance
- (b) The total current flowing

$$I = \frac{V}{R} = \frac{12}{\quad}$$

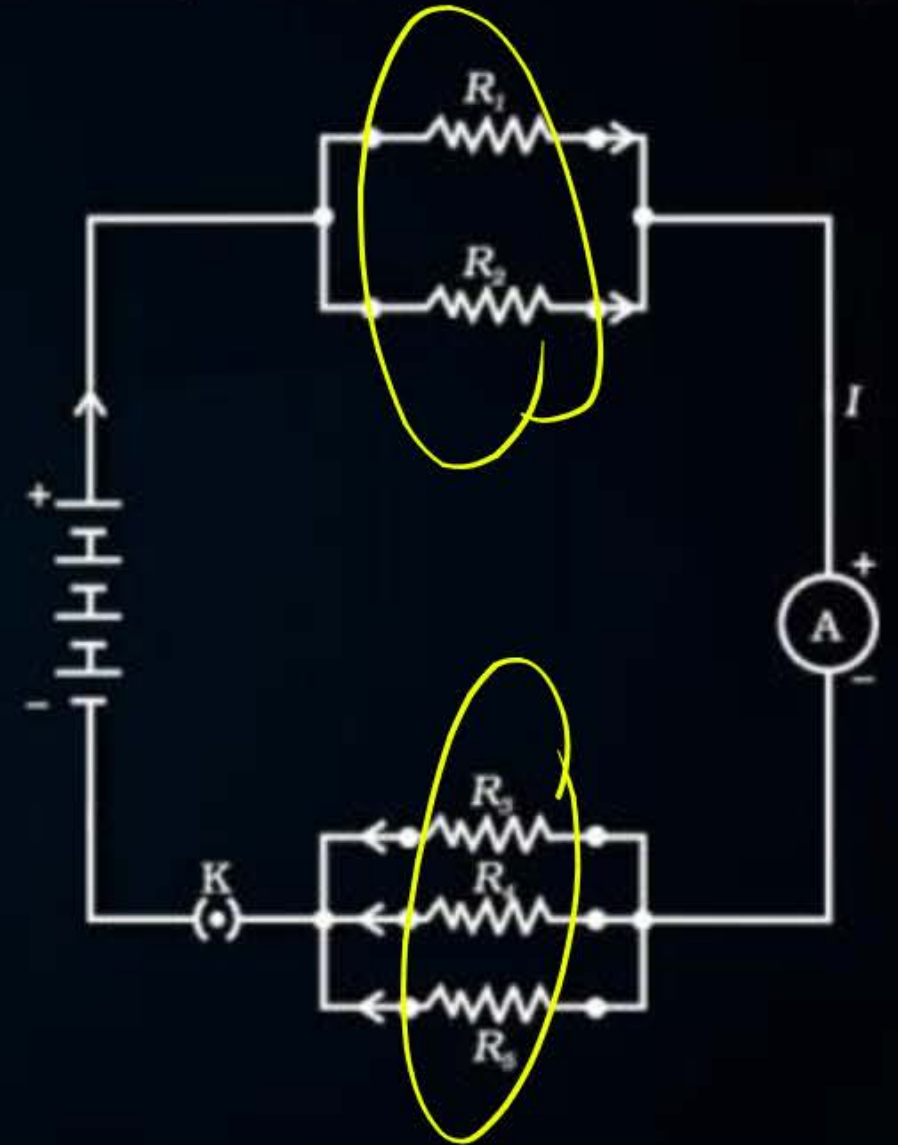




# RESISTANCE OF AMMETER AND VOLTMETER



## Ideal Ammeter

$$R = 0 \Omega$$


'Series device'

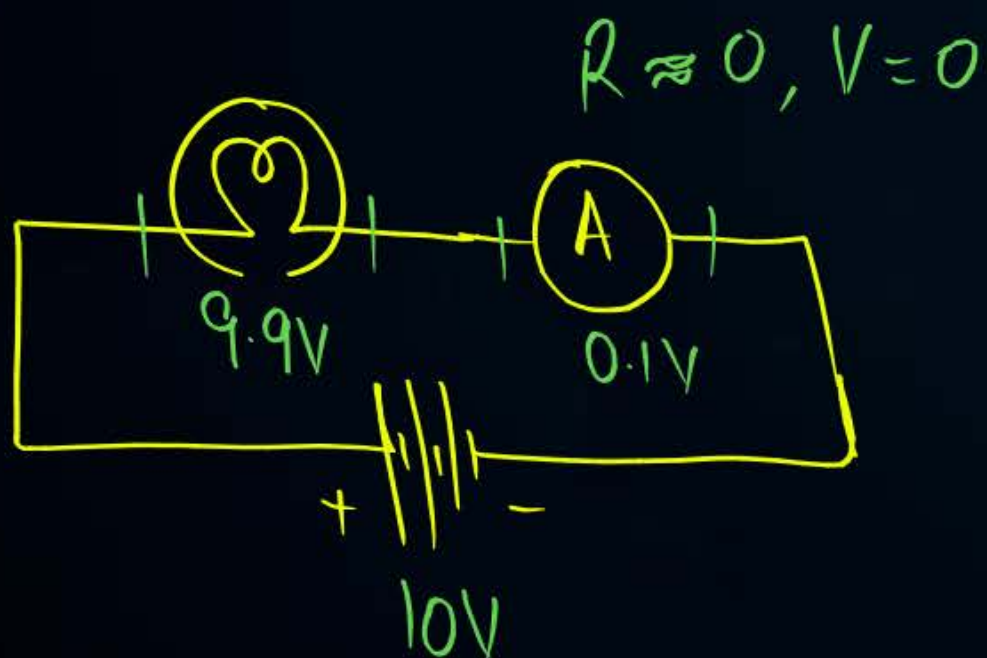

## Ideal Voltmeter

$$R = \infty$$

'Parallel Device'

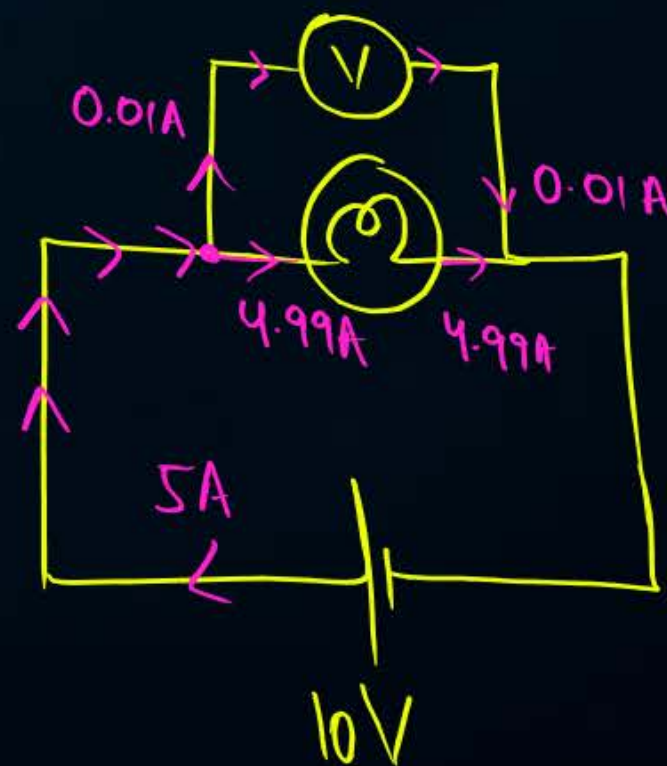


$R \Rightarrow$  Very high





# WORKING OF RHEOSTAT

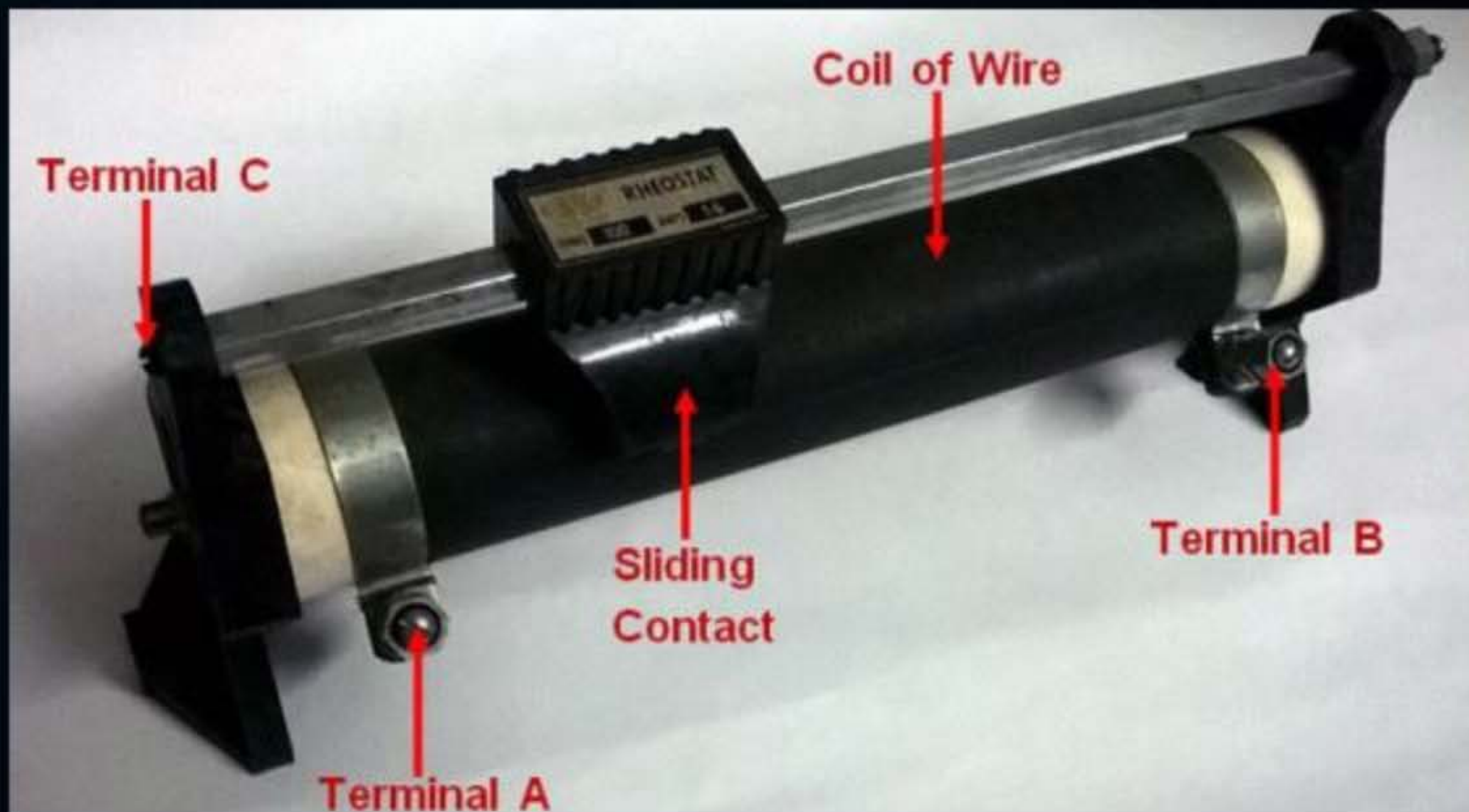



THANK  
YOU

