

## UDAAN 2025

## PHYSICS

DHA : 07

## ELECTRICITY

**Q1** The formula for Ohm's law is

- (A)  $I = V/R$
- (B)  $V = IR$
- (C)  $R = V/I$
- (D) All are correct

**Q2** According to Ohm's Law, what is the current (I) when 500 Voltage (V) is supplied to a 2K Resistance (R)?

- (A) 0.50 Amp
- (B) 0.25 Amp
- (C) 0.75 Amp
- (D) 4 Amp

**Q3** A cooler of 1500 W, 200 volts and a fan of 500 W, 200 volts are to be used from a household supply. The rating of the fuse to be used is

- (A) 2.5 A
- (B) 5.0 A
- (C) 7.5 A
- (D) 10 A

**Q4** In an electrical circuit, two resistors of  $2\ \Omega$  and  $4\ \Omega$ , respectively, are connected in series to a 6 V battery. The heat dissipated by the  $4\ \Omega$  resistor in 5 s will be

- (A) 5 J
- (B) 10 J
- (C) 20 J
- (D) 30 J

**Q5** A lamp is connected to a battery. The current in the lamp is 0.32 A. The charge of an electron is  $1.6 \times 10^{-19}\text{C}$ . How many electrons flow through the lamp in 1 min ?

- (A)  $1.2 \times 10^{19}$
- (B)  $1.2 \times 10^{20}$
- (C)  $1.2 \times 10^{21}$
- (D)  $1.2 \times 10^{21}$

**Q6** Which is a unit of current?

- (A)  $\text{CV}^{-1}$
- (B) Cs
- (C)  $\text{Cs}^{-1}$
- (D) CV


**Q7** An electric charge on a body produces:

- (A) a magnetic field only
- (B) an electric field only
- (C) both electric and magnetic field
- (D) neither electric nor magnetic field

**Q8** If a charged body attracts another body, the charge on the other body:

- (A) must be negative
- (B) must be positive
- (C) must be zero
- (D) may be negative or positive

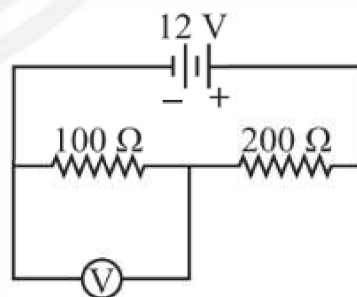**Q9** In the circuit shown in figure. The reading of the voltmeter V will be




- (A) 4 V
- (B) 2 V
- (C) 6 V
- (D) 3 V


**Q10** Which of the following networks yields maximum effective resistance between A and B




(A)

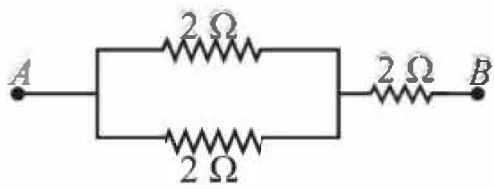


(B)

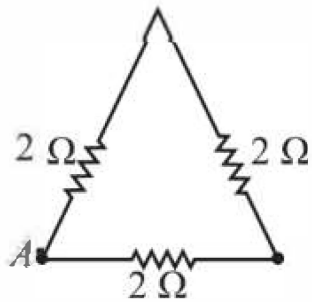

(C)

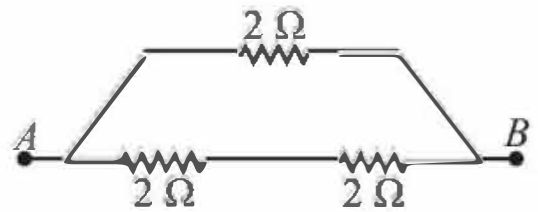

(D)

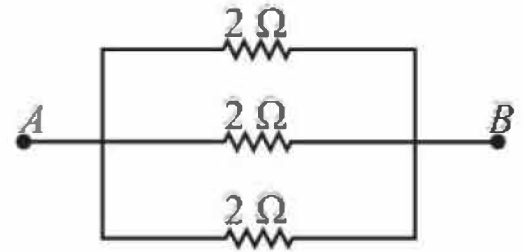

## Answer Key

Q1 (D)

Q2 (B)

Q3 (D)

Q4 (C)

Q5 (B)

Q6 (C)

Q7 (B)

Q8 (D)

Q9 (A)

Q10 (A)



[Android App](#)

|

[iOS App](#)

|

[PW Website](#)

# Hints & Solutions

**Q1 Text Solution:**

where V is voltage, I is current and R is resistance

**Video Solution:**

**Q2 Text Solution:**

$V=IR$  is used to solve

**Video Solution:**

**Q3 Text Solution:**

$I = P/V$

**Video Solution:**

**Q4 Text Solution:**

Find the equivalent resistance of the Circuit,

Find the current through  $4\Omega$  resistor, Heat dissipated through  $4\Omega$  resistor by  $H = I^2 RT$

**Video Solution:**

**Q5 Text Solution:**

Use  $Q = It = ne$

**Video Solution:**

**Q6 Text Solution:**

$$\text{Current (I)} = \frac{Q}{t} = \frac{C}{S} = CS^{-1}$$

**Video Solution:**

**Q7 Text Solution:**

Charge at rest produces only electric field.

**Video Solution:**

**Q8 Text Solution:**

Two oppositely charged bodies attract each other.

**Video Solution:**

**Q9 Text Solution:**

Find current across  $100\Omega$  resistance and then use formula  $[V = IR]$  for finding the voltmeter reading.



**Video Solution:**



**Q10 Text Solution:**

Use concept of series and parallel combination of resistance.

**Video Solution:**



[Android App](#)

| [iOS App](#)

| [PW Website](#)

