

UPDAAN

2025

ELECTRICITY

PHYSICS

Lecture - 05

By - ER. RAKSHAK SIR



Topics to be covered



- 1 SERIES CIRCUIT ✓
 - 2 PARALLEL CIRCUIT ✓
 - 3 COMBINATION OF RESISTORS ✓
 - 4 RESISTANCE OF AMMETER AND VOLTMETER
 - 5 WORKING OF RHEOSTAT
- } Derivation




* Revision (OP)

1) Charge

$$Q = ne$$

net charge \swarrow no. of electrons \searrow electronic charge \downarrow
 $1.6 \times 10^{-19} \text{ C}$

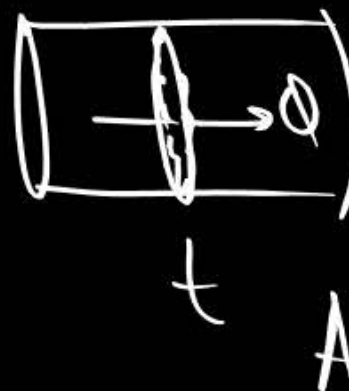2) Current = $\frac{\text{Amount of charge}}{\text{time}}$



$$I = \frac{Q}{t}$$

3) Voltage = $\frac{\text{Workdone}}{\text{Charge}}$

$$V = \frac{W}{Q}$$

Volts \swarrow Joule \searrow Coulomb \searrow


4) Ohm's Law

1) Conductor (ohmic)

2) $T = \text{constant}$


$$V \propto I$$

$$V = IR$$

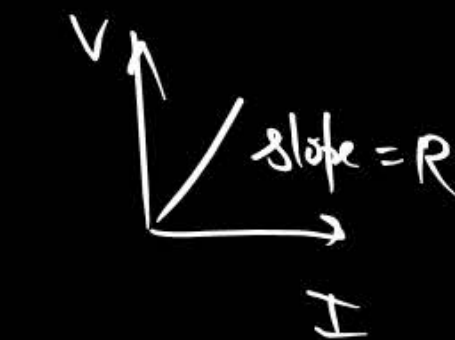

Const.


5) Resistance (Ω)

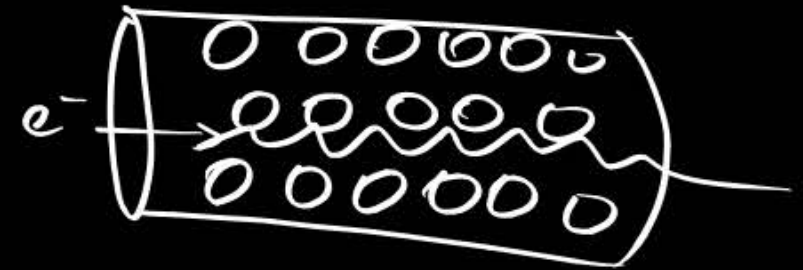

$$R = \rho \frac{l}{A}$$

$R \propto l$
 $R \propto \frac{1}{A}$
 Const. (Material)

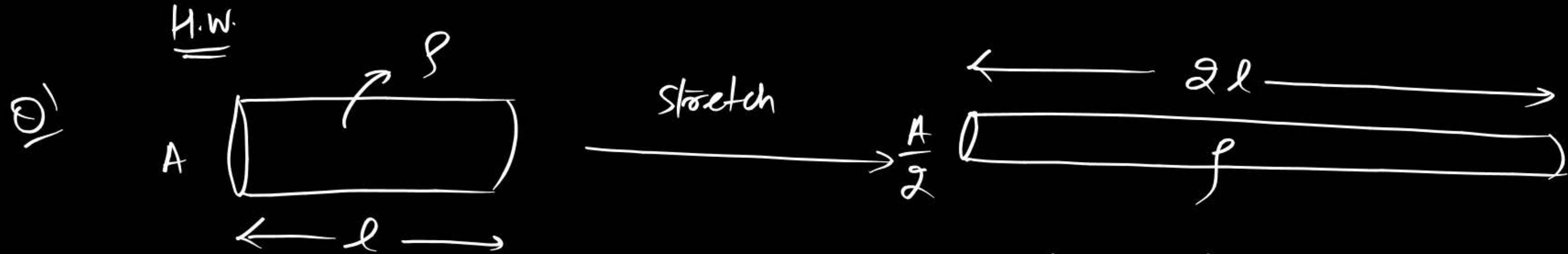6) $\rho \rightarrow$ Material depend
 \rightarrow Ohm-metre
 $\rightarrow T \uparrow \rho \uparrow$



a) $R = \rho \frac{l}{A}$

$$R' = \rho \frac{2l}{\frac{A}{2}} = 4 \left(\rho \frac{l}{A} \right)$$

$$\boxed{R' = 4R}$$

Ans - New Resistance is 4 times the old one.

b) $\rho \Rightarrow$ No change

Q2 Resistance of a wire becomes 8 times :-

hint :-

~~A)~~ $l \rightarrow \text{double} : R \rightarrow \text{double}$

~~B)~~ $l \rightarrow \text{triple} : R \rightarrow \text{triple}$



C) $R \rightarrow \text{double}$
 $l \rightarrow \text{double}, r \rightarrow \text{half}$
 $A \rightarrow \frac{1}{4}A$

$R' = \rho \frac{l}{A}$
 $D) l \rightarrow \text{half}, r \rightarrow \text{double}$
 $R \rightarrow \text{half}, A \rightarrow 4 \text{ times}$
 $R' = \rho \frac{\frac{l}{2}}{4A} = \frac{\rho l}{8A} = \frac{1}{8} \left(\rho \frac{l}{A} \right)$
 $R' = \frac{R}{8}$

$$R' = \rho \frac{2l}{\frac{1}{4}A}$$

$$R' = 8 \left(\rho \frac{l}{A} \right)$$

$$R' = 8R$$

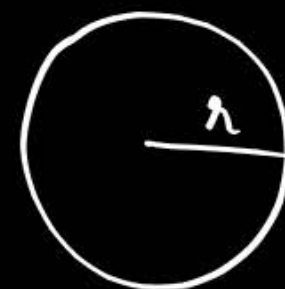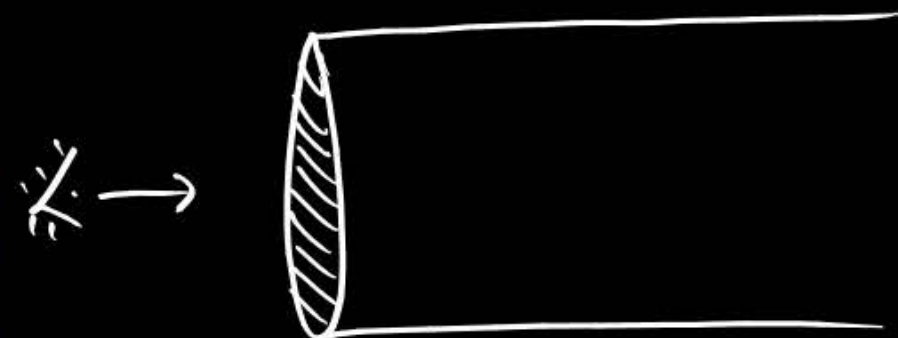

$$A = \pi r^2$$

$$l \rightarrow 3l$$

$$A \rightarrow 9A$$

$$r \rightarrow 2r$$


$$A \rightarrow 4A$$

$$r \rightarrow \frac{1}{2}r$$


$$A \rightarrow \frac{1}{4}A$$

Series

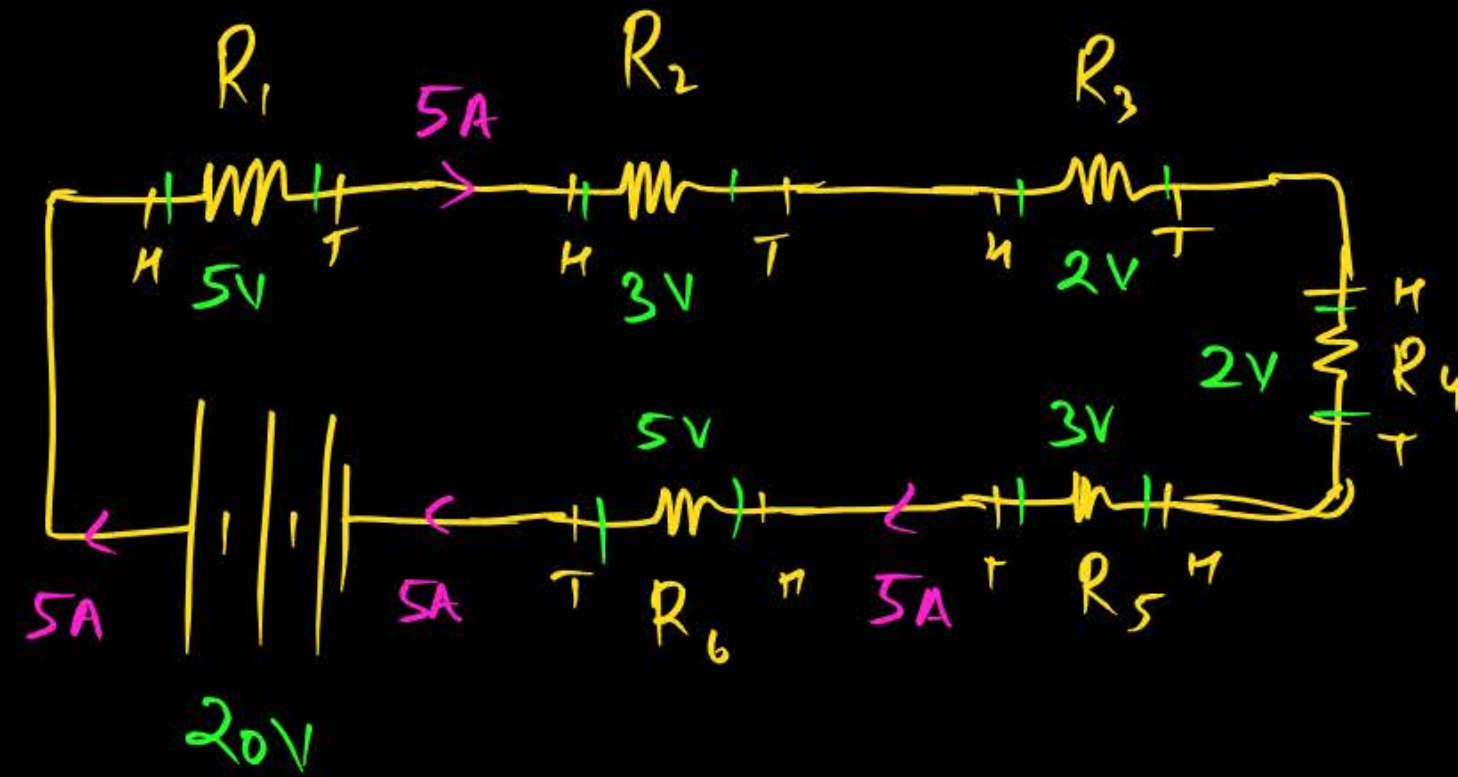- Head-tail connection
- Only one branch (wire)
Ka Connection



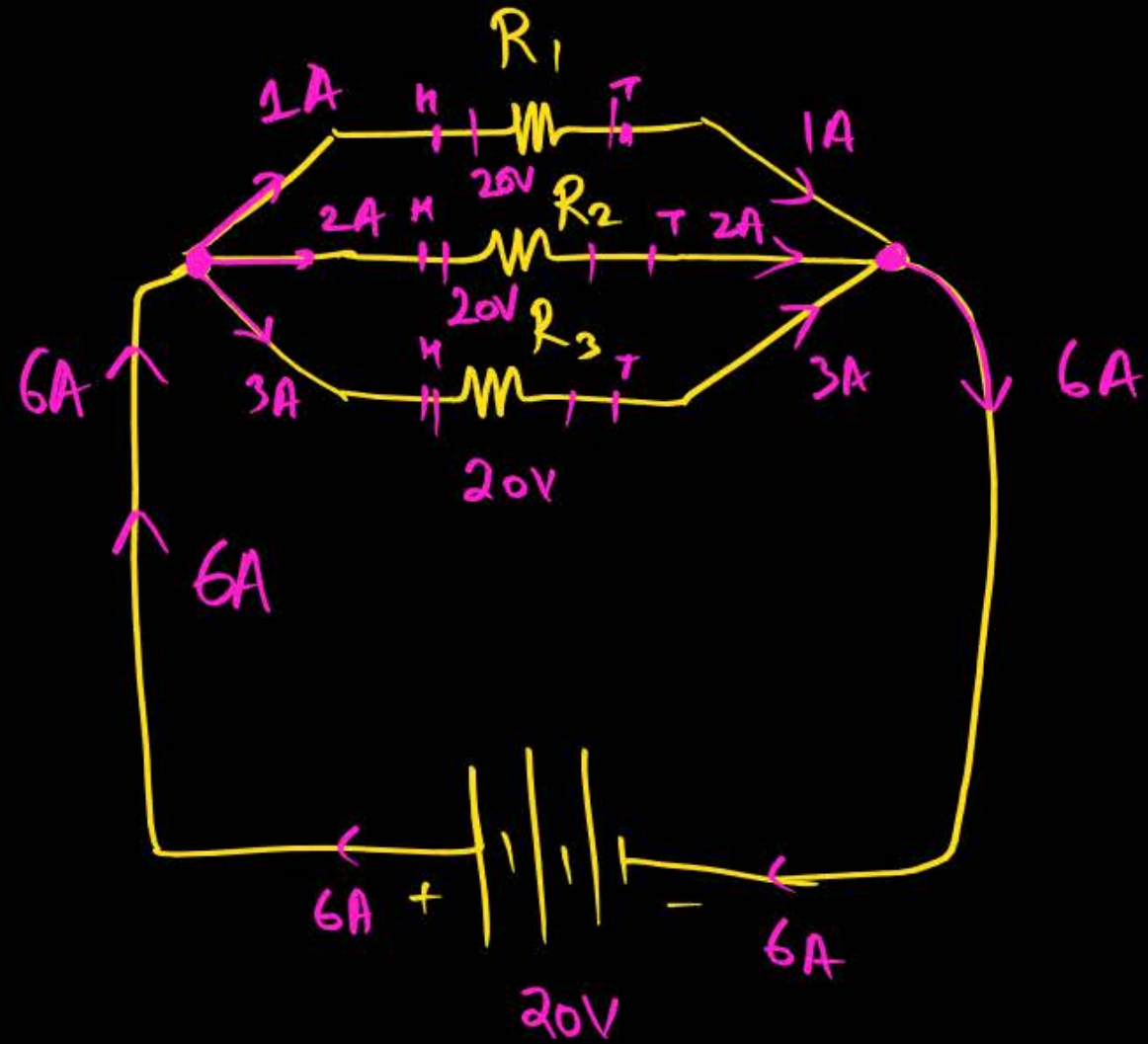
- Kyuki Path same
Toh Current Bhi Same
- Voltage divides in a Series
Circuit.



Parallel

→ Head-head or Tail-Tail connection

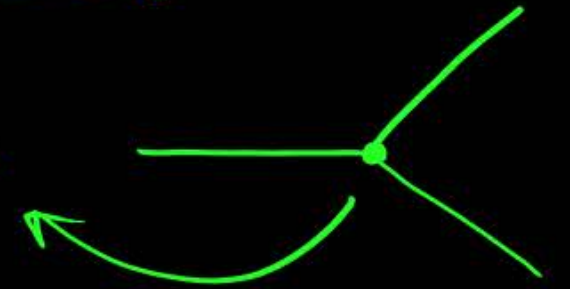→ Wire joints are visible
or
Nodes/Junctions



→ Path divides
Current divides

→ Voltage same



SERIES CIRCUIT

$I = \text{Same}$
 $V = \text{divide}$



* Derivation :-

$$V_t = V_1 + V_2 + V_3$$



Applying ohm's Law ($V = IR$)

$$IR_t = IR_1 + IR_2 + IR_3$$

$$R_t = R_1 + R_2 + R_3$$

Net / Total / effective / equivalent

$$R_t = R_1 + R_2 + R_3$$

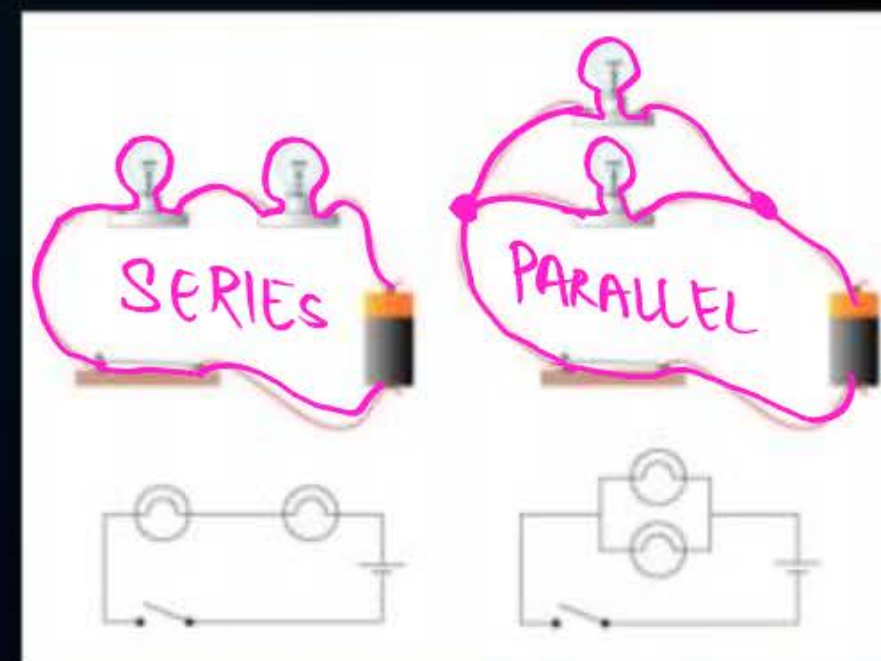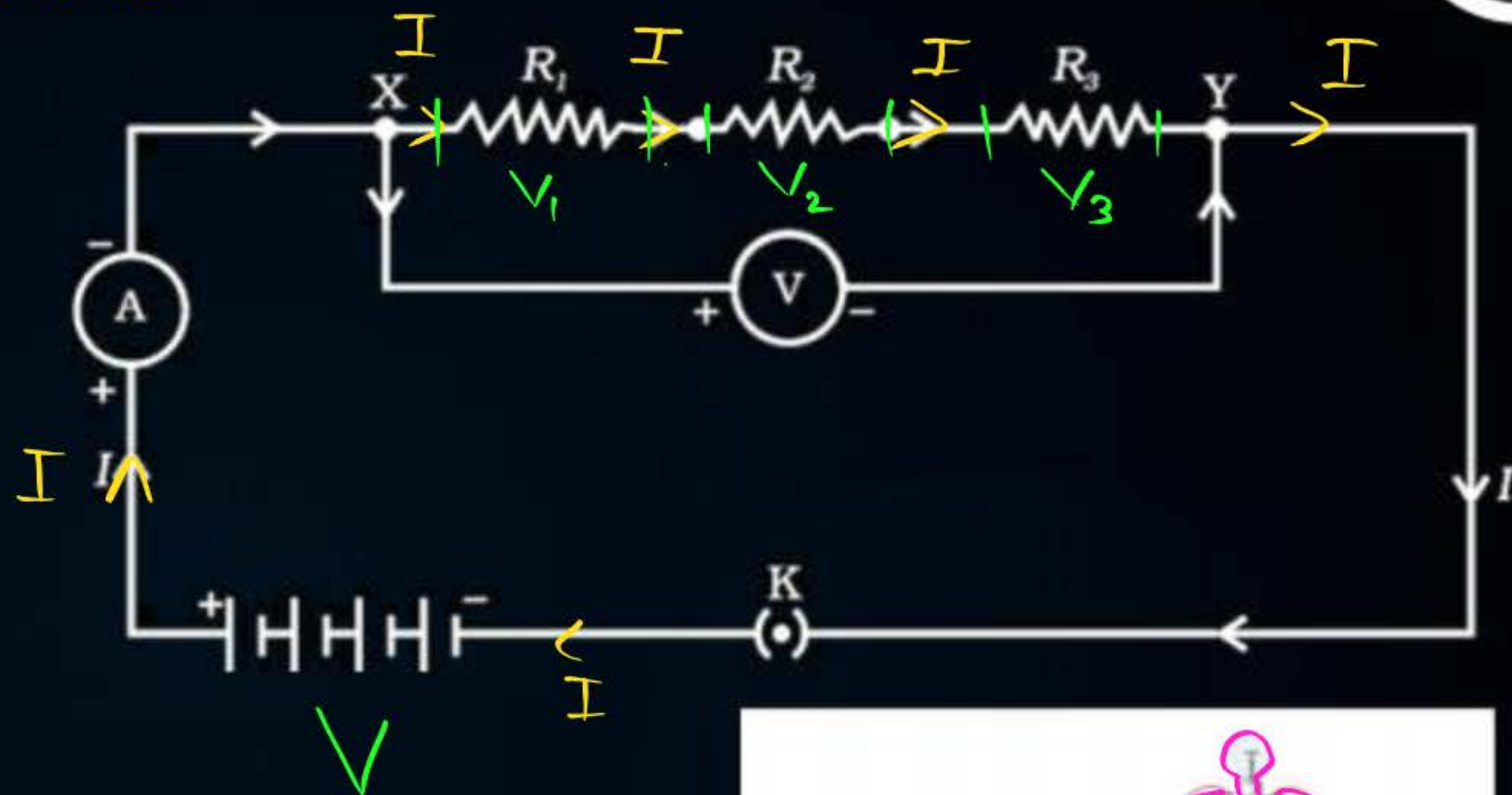



PARALLEL CIRCUIT

$I = \text{divide}$
 $V = \text{Same}$



* Derivation :-

$$I_t = I_1 + I_2 + I_3$$


Applying ohm's law $V = IR$
 $I = \frac{V}{R}$

$$\frac{V}{R_t} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{V}{R_t} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

\Rightarrow
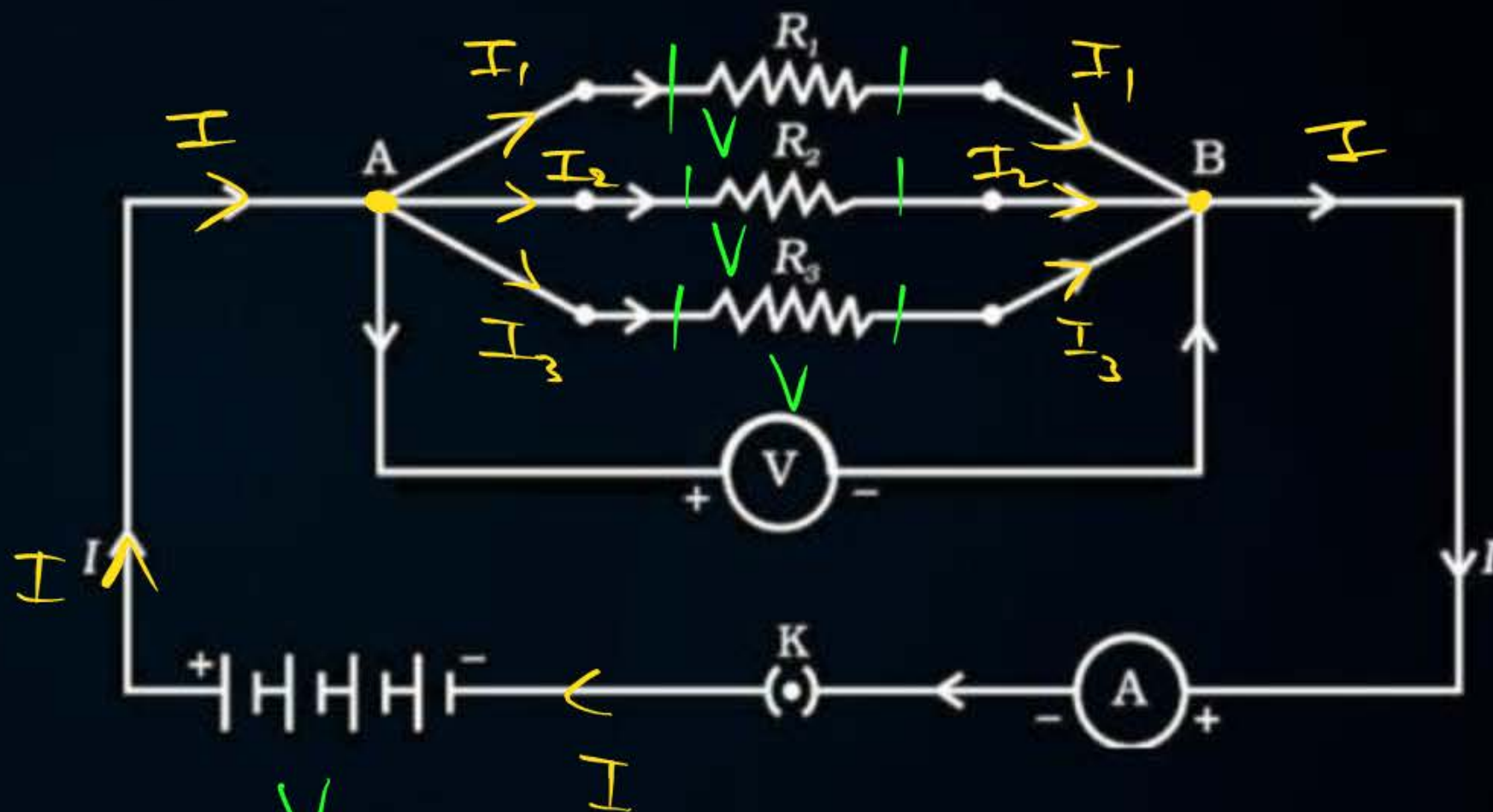
$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$





COMBINATION OF RESISTORS



Series:


$$R_1 = 3\Omega \quad R_2 = 2\Omega \quad R_3 = 5\Omega$$

Level-I



$$\begin{aligned} R_t &= R_1 + R_2 + R_3 = 2 + 3 + 5 = 10\Omega \\ R_t &= 10\Omega \end{aligned}$$

Level-II

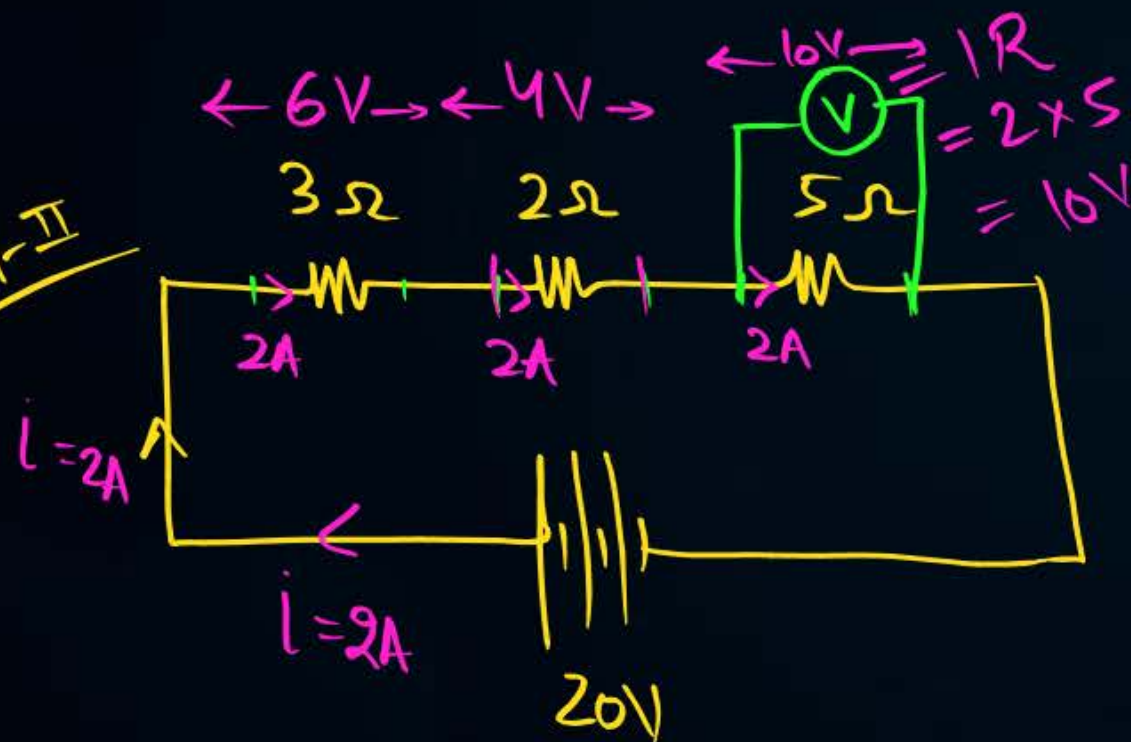

find the current drawn in the circuit \Rightarrow ?

$$R_t = 10\Omega, \quad V = 20V$$

$$i = \frac{V}{R} = \frac{20}{10} = 2A \checkmark$$

Level-III

$$\text{find } V_{\text{at } 5\Omega} = iR = 2 \times 5 = 10V$$




COMBINATION OF RESISTORS



$I = \text{divide}$

Parallel: $V = \text{Same}$

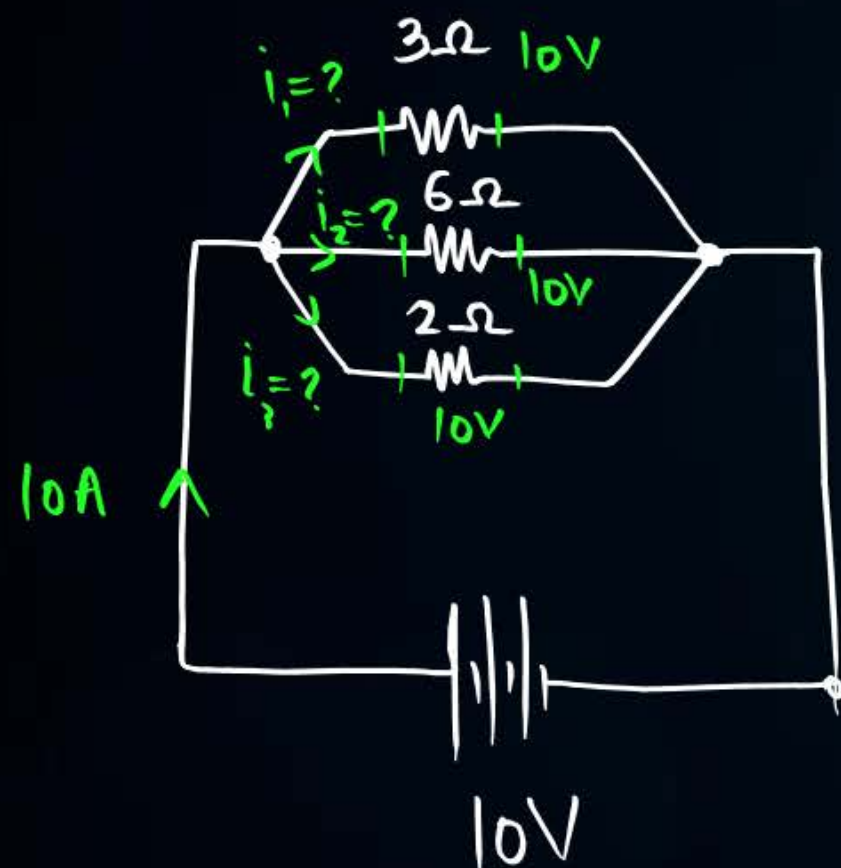

level-1 find $R_t = ?$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_t} = \frac{1}{3} + \frac{1}{6} + \frac{1}{2} = \frac{4+2+6}{12} = \frac{12}{12} = 1$$

Level-2

find $I = ?$

$$R_t = 1\Omega \quad \checkmark$$

$$V = IR$$

$$10 = I \times 1$$

$$I = 10A \quad \checkmark$$

level-3

find




$$i_1 = \frac{V}{R_1} = \frac{10}{3} = 3.33A$$

$$i_2 = \frac{V}{R_2} = \frac{10}{6} = \frac{5}{3} = 1.66A$$



$$i_3 = \frac{V}{R_3} = \frac{10}{2} = 5A$$

PRACTICE PROBLEMS 1:

TRICKS (for MCQ or Answer Jhatka Verify)

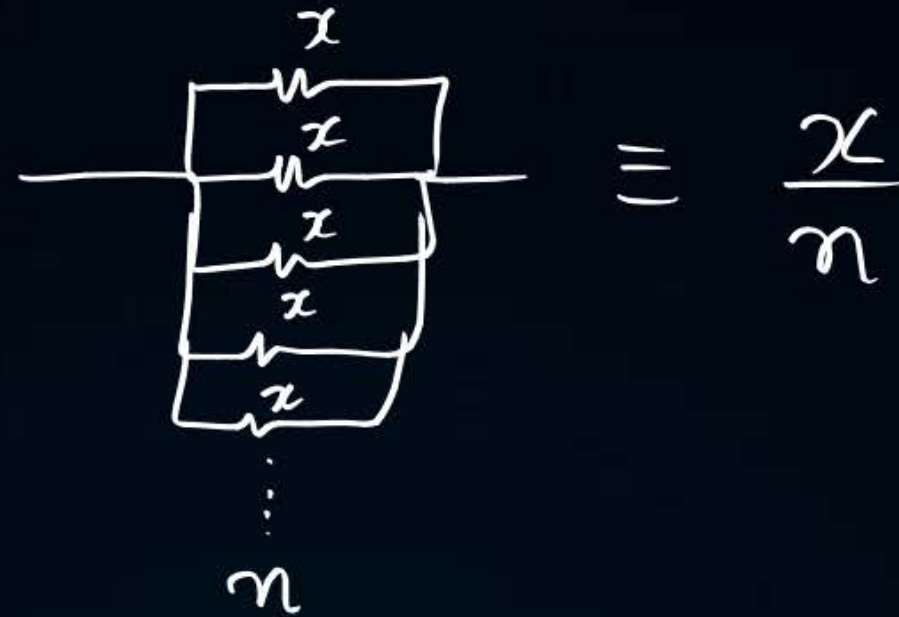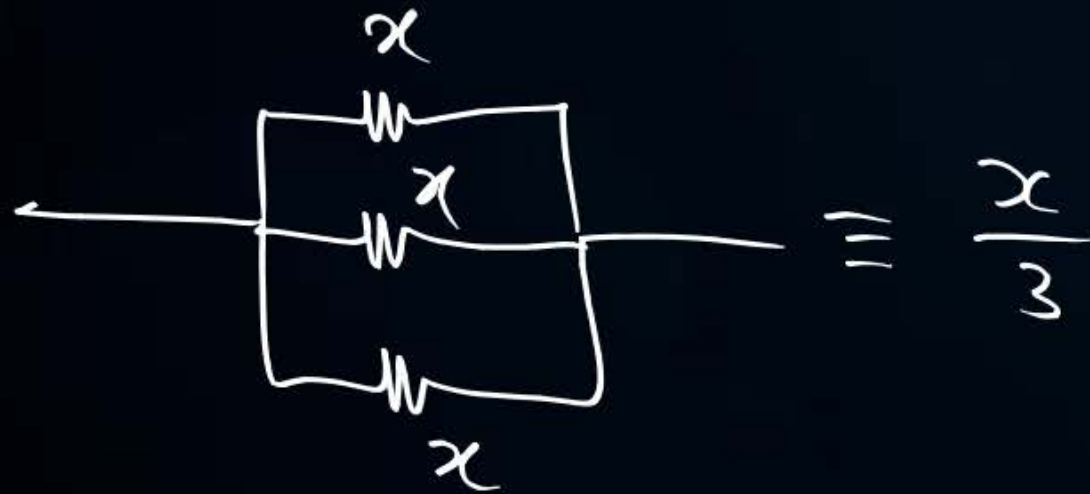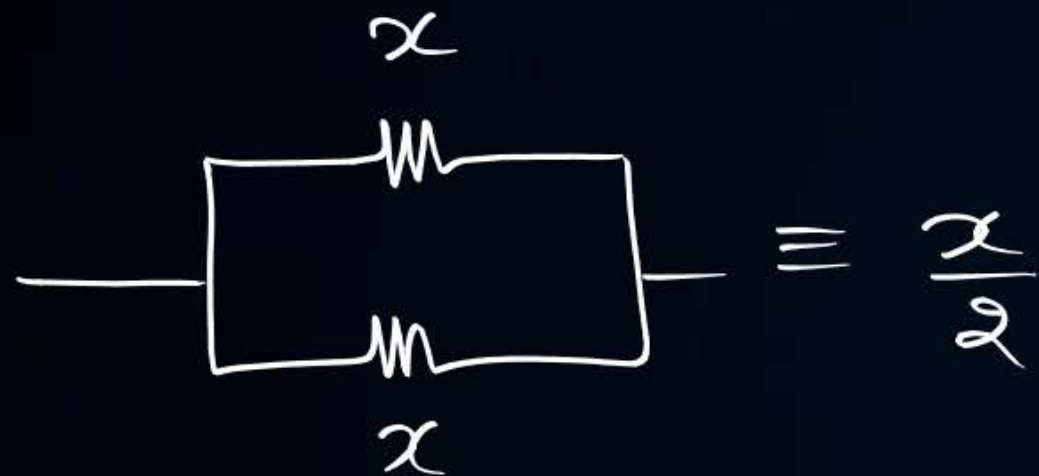

Common

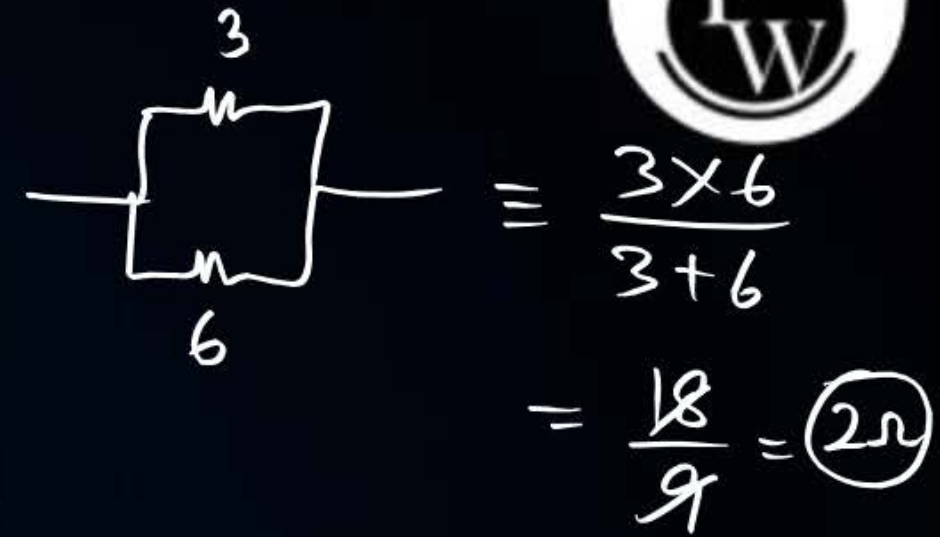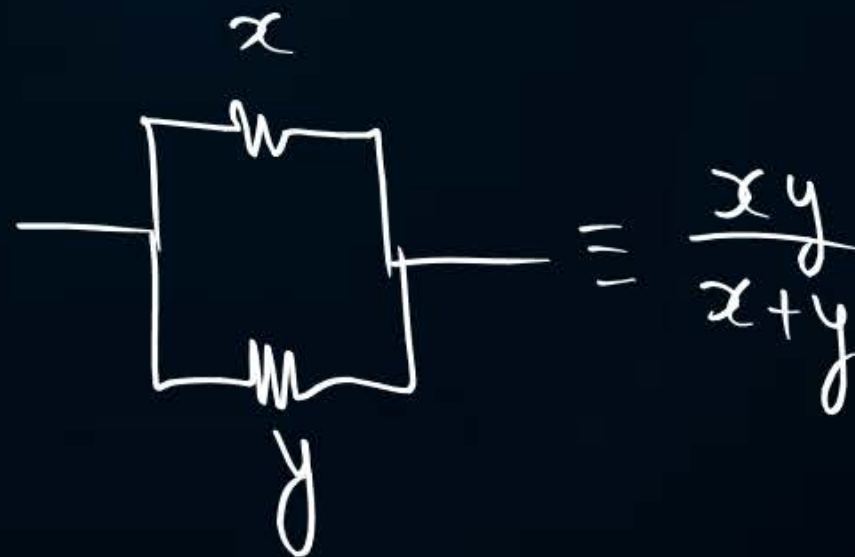

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_t} = \frac{1}{3} + \frac{1}{6} = \frac{2+1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$\frac{1}{R_t} = \frac{1}{2} \Rightarrow R_t = 2\Omega$$






Imp.
Ques



↓ divides it into

5 equal parts

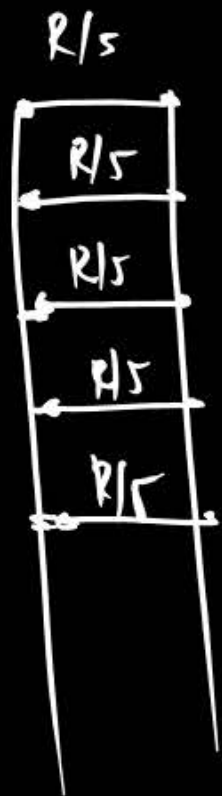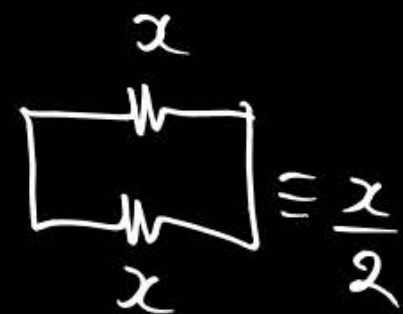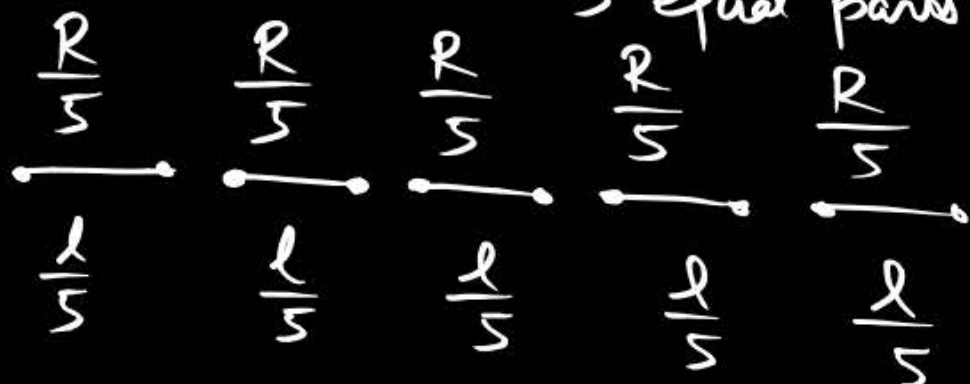

$$\equiv \frac{R/5}{5} = \left(\frac{R}{25} \right) \checkmark$$

R

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$

$$\frac{1}{R_t} = \frac{1}{\frac{R}{5}} + \frac{1}{\frac{R}{5}} + \frac{1}{\frac{R}{5}} + \frac{1}{\frac{R}{5}} + \frac{1}{\frac{R}{5}}$$


$$\frac{1}{R_t} = \frac{5}{R} + \frac{5}{R} + \frac{5}{R} + \frac{5}{R} + \frac{5}{R}$$

$$\frac{1}{R_t} = \frac{25}{R}$$

$$R_t = \frac{R}{25}$$


$$\frac{R_{\text{Pehle}}}{R_{\text{Baad}}} = \frac{R}{\frac{R}{25}} = 25 \frac{R}{R}$$

$$R : R' = 25 : 1$$

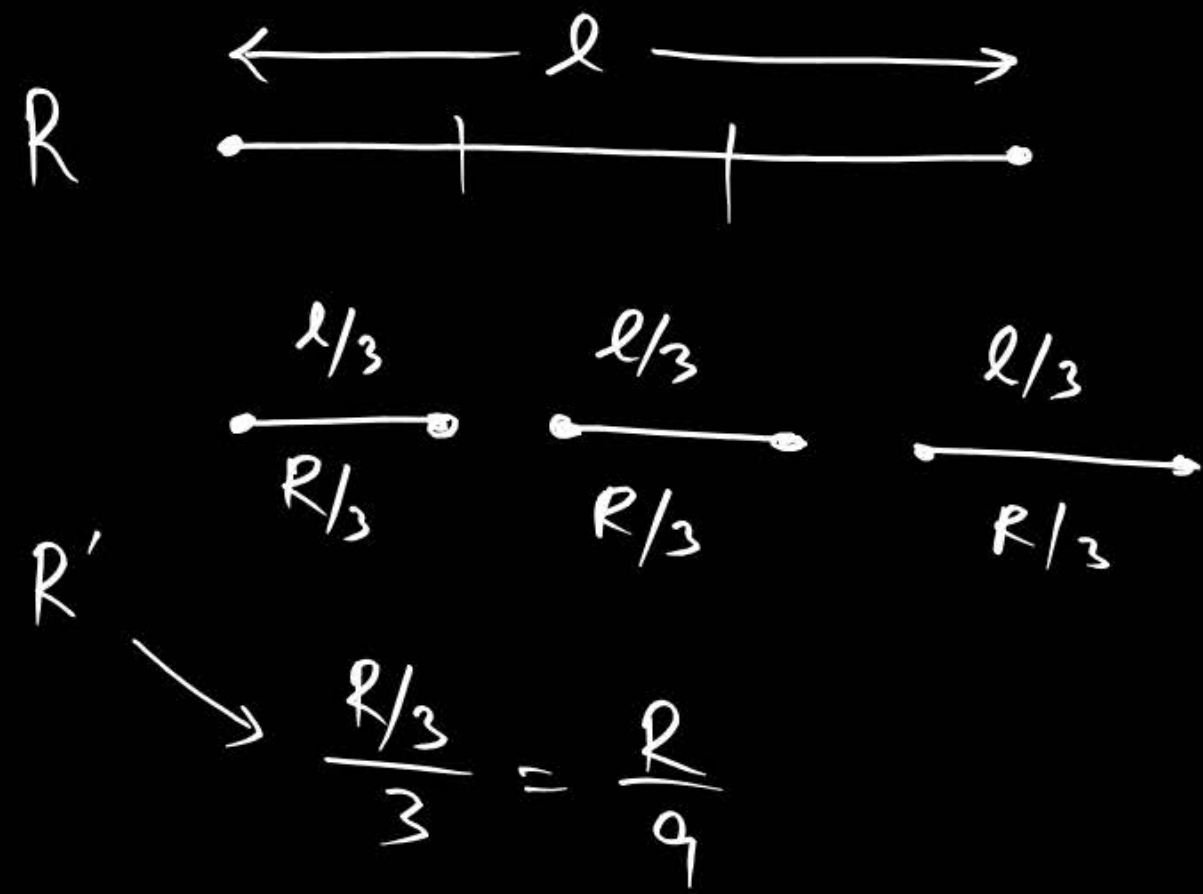

$$R : R' = R : \frac{R}{9} = 1 : \frac{1}{9} = \boxed{9 : 1}$$

General Jugaad (Ge Ju)

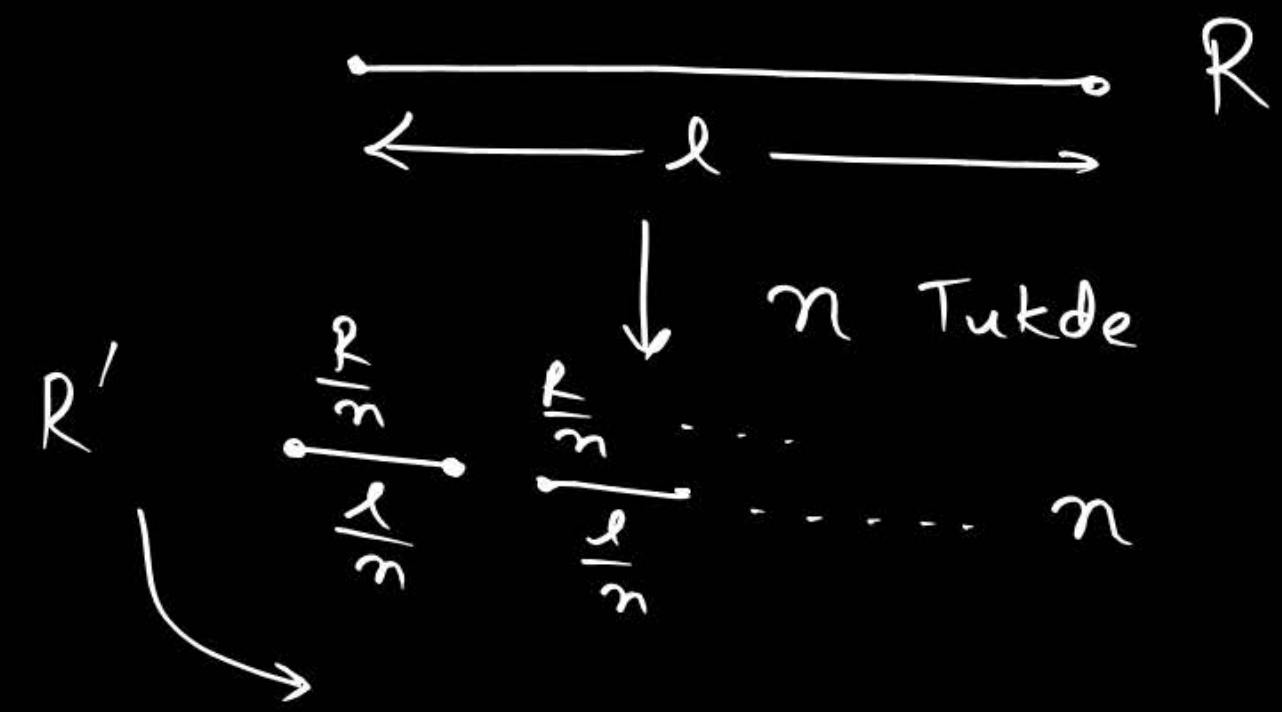

$$R : R' = n^2 : 1$$

↓ ↓
Pahle Baad

QUESTION

H.W.



A piece of wire of resistance R is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R' , then the ratio R/R' is:

A $1/25$

B $1/5$

C 5

D 25

QUESTION

H.W.



How many $176\ \Omega$ resistors (in parallel) are required to carry $5\ A$ on a $220\ V$ line?



THANK
YOU

