



**PHYSICS**

# **ELECTRICITY**

**ONE SHOT**

**Lecture No.- 05**



**ER. RAKSHAK SIR**

# Today's Targets



NCERT DISCUSSION



What does an electric circuit mean?

→ refer Notes





Define the unit of current.

$$\rightarrow \text{Ampere} = \frac{\text{Coulomb}}{\text{Second}}$$

When 1C of charge is transferred in 1 sec  
Current is said to be 1A.

Calculate the number of electrons constituting one coulomb of charge.

 $n$  $Q = 1\text{C}$ 

$$Q = ne$$

$$1 = n \times 1.6 \times 10^{-19}$$

$$n = \frac{1}{1.6 \times 10^{-19}}$$

$$= \frac{10^6 \times 10^{19}}{1.6}$$

$$= \frac{10^{25}}{16} = 6.25 \times 10^{18}$$

$$= 6.25 \times 10^{18}$$

↓  
1C



Name a device that helps to maintain a potential difference across a conductor.

→ Battery



What is meant by saying that the potential difference between two points is 1 V?

$$V = \frac{W}{Q}$$

\* 
$$1V = \frac{1J}{1C}$$

When 1J of work is done  
on 1C of charge, p.d. is 1V.



How much energy is given to each coulomb of charge passing through a 6 V battery?

$$\left. \begin{array}{l} V = 6V \\ Q = 1C \\ W = E = ? \end{array} \right\}$$

$$V = \frac{W}{Q}$$

$$6 = \frac{W}{1}$$

$$W = 6J \quad \checkmark$$



On what factors does the resistance of a conductor depend?



$$R = \rho \frac{l}{A}$$

- 1) length ( $l$ )  $\uparrow R \uparrow$
- 2) Cross-sectional Area ( $A$ )  $\uparrow R \downarrow$
- 3) Material  $\rho \uparrow R \uparrow$
- 4) Temperature  $\uparrow R \uparrow$



Will current flow more easily through a thick wire or a thin wire of the same material, when connected to the same source? Why?

 $A \uparrow$  $A \downarrow$  $V$  $\rho$  $\Rightarrow I \uparrow$ 

$$R \downarrow = \rho \frac{L}{A} \uparrow$$

Thick wire has more cross-sectional Area, its Resistance with the same voltage source is less and current flows more easily

 $A \uparrow R \downarrow \rho = \text{same } I \uparrow$



Let the resistance of an electrical component remains constant while the potential difference across the two ends of the component decreases to half of its former value. What change will occur in the current through it?

$$R = \text{Constant}$$

$$V = V$$

$$I = I$$

$$V = IR$$

$$\frac{V}{I} = R$$

$$V' = \frac{V}{2}$$

$$I' = ?$$

$$R = \text{const.}$$

$$V' = I'R$$

$$\frac{V}{2} = I'R$$

$$\frac{V}{2} = I' \frac{V}{I}$$

$$\frac{I}{2} = I' \quad \text{Ans}$$



Why are coils of electric toasters and electric irons made of an alloy rather than a pure metal?

⇒ Nichrome Alloy  
J ↑ R ↑ H ↑

Homogenous Mixture  
of Metals & non-Metals

H.W.

Use the data in Table 12.2 to answer the following –


- (a) Which among iron and mercury is a better conductor?
- (b) Which material is the best conductor?

P↓

P↓↓



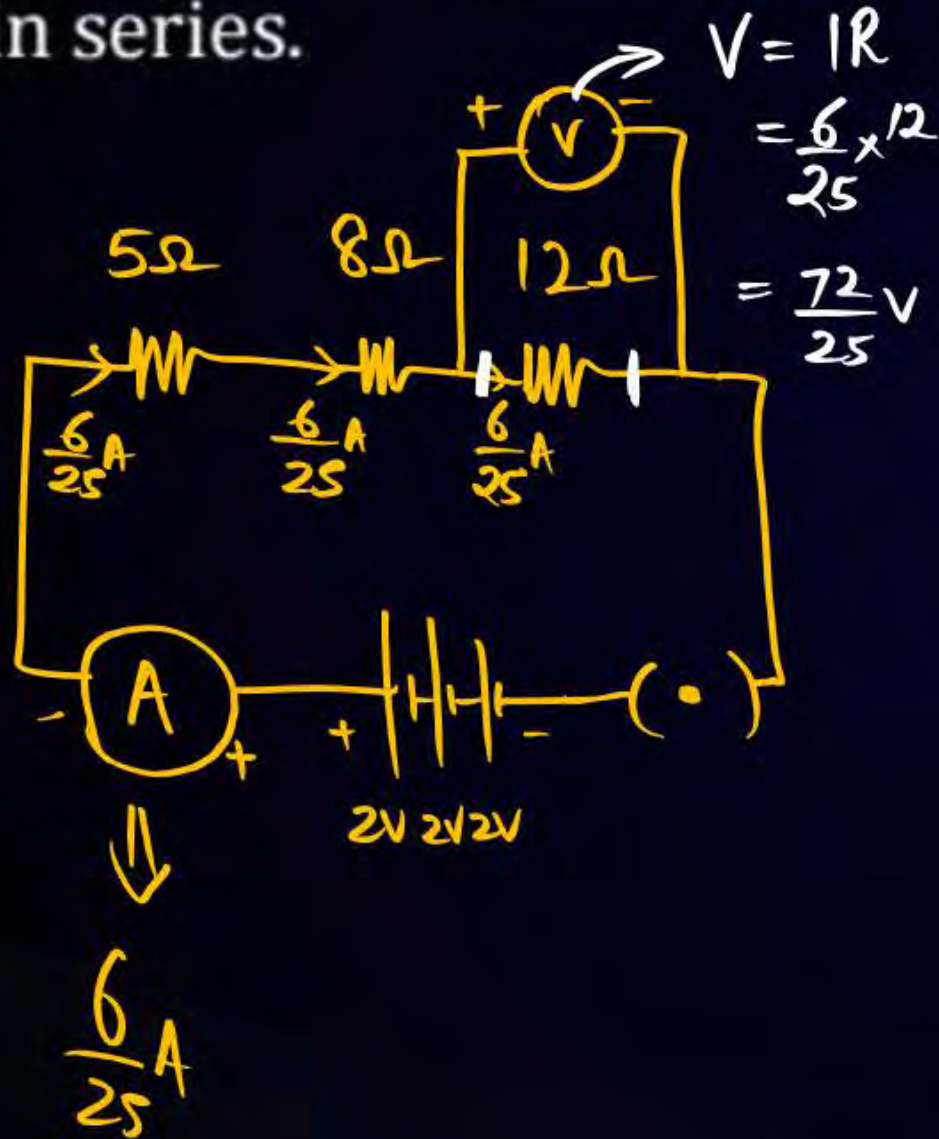Draw a schematic diagram of a circuit consisting of a battery of three cells of 2 V each, a  $5\ \Omega$  resistor, an  $8\ \Omega$  resistor, and a  $12\ \Omega$  resistor, and a plug key, all connected in series.




$$V = IR$$
$$6 = I \times 25$$

$$I = \frac{6}{25}A$$




Redraw the circuit of Question 1, putting in an ammeter to measure the current through the resistors and a voltmeter to measure the potential difference across the  $12\ \Omega$  resistor. What would be the readings in the ammeter and the voltmeter?

P.T.P.

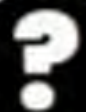

Judge the equivalent resistance when the following are connected in parallel -

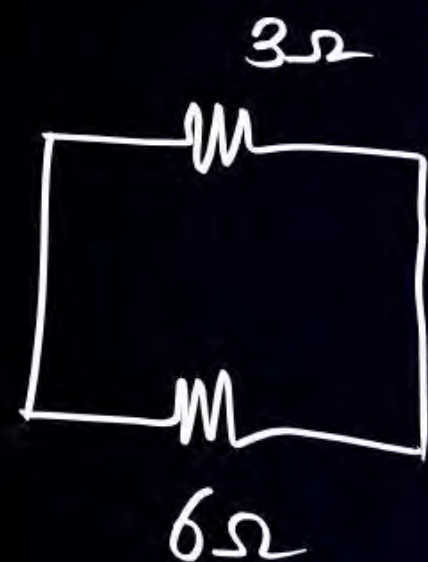(a)  $1 \Omega$  and  $10^6 \Omega$ , (b)  $1 \Omega$  and  $10^3 \Omega$ , and  $10^6 \Omega$ .  $\approx 1 \Omega$



$= 2 \Omega$





$$\frac{1}{R_t} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6}$$

$$\frac{1}{R_t} = \frac{3+2+1}{6} = \frac{6}{6} = 1$$

$$R_t = 1 \Omega$$



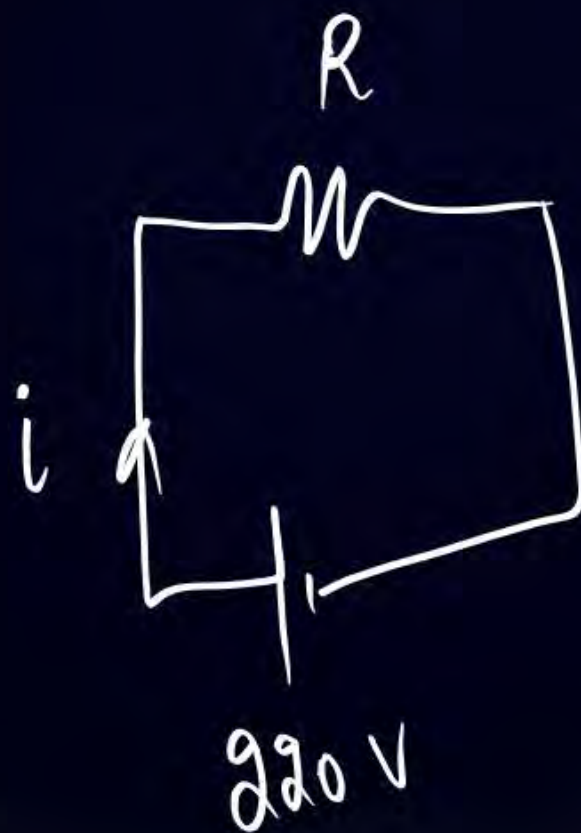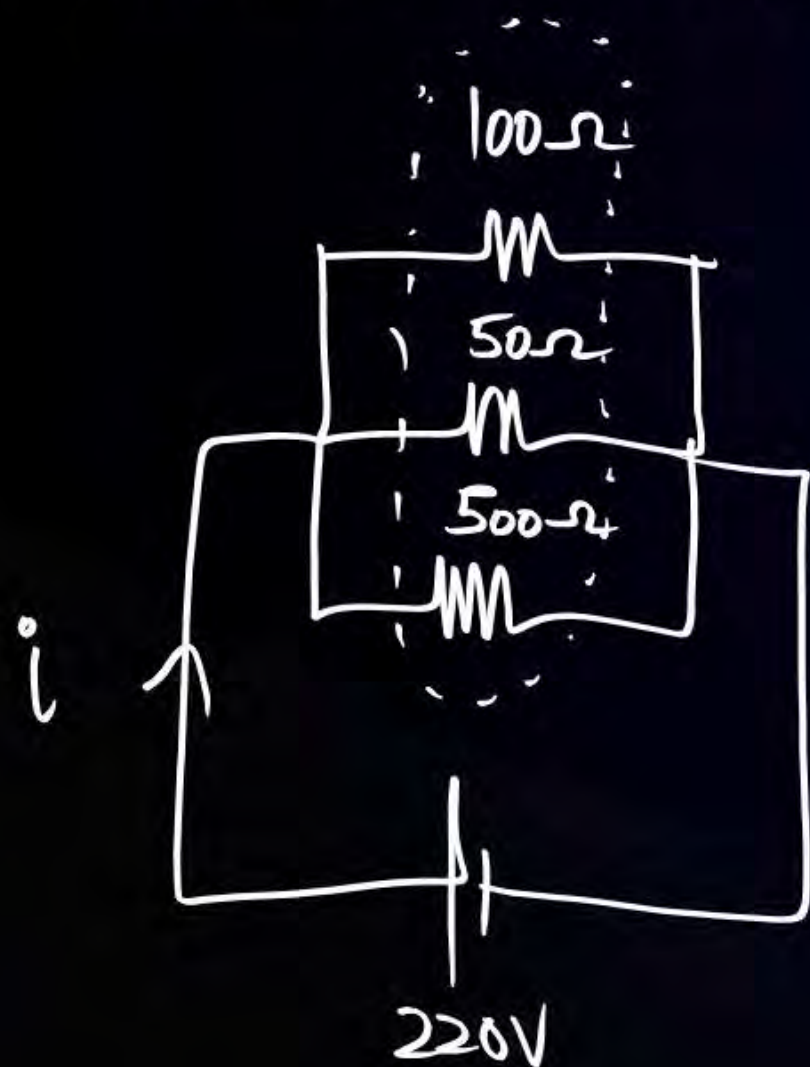An electric lamp of  $100\ \Omega$ , a toaster of resistance  $50\ \Omega$ , and a water filter of resistance  $500\ \Omega$  are connected in parallel to a  $220\text{ V}$  source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances, and what is the current through it?



$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{50} + \frac{1}{100} + \frac{1}{500}$$

$$= \frac{10 + 5 + 1}{500} = \frac{16}{500}$$

$$R_t = \frac{500}{16}\ \Omega \Rightarrow I_{\text{iron}}$$




What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?  $\checkmark$

- 1) Voltage remains same, each appliance works on full efficiency.
- 2) Each appliance gets a separate switch.
- 3) If one appliance gets damaged, other work properly.


How can three resistors of resistances  $2\ \Omega$ ,  $3\ \Omega$ , and  $6\ \Omega$  be connected to give a total resistance of (a)  $4\ \Omega$ , (b)  $1\ \Omega$ ?




$\times$    $= 11\ \Omega$   $\times$

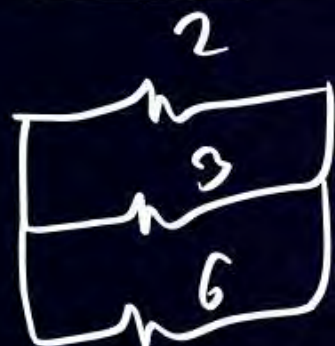
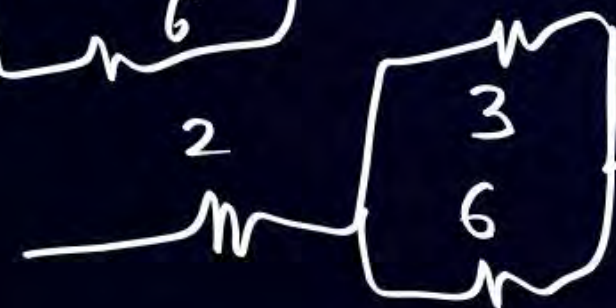
$$\frac{1}{R_t} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6} = \frac{3+2+1}{6} = \frac{6}{6} = 1$$


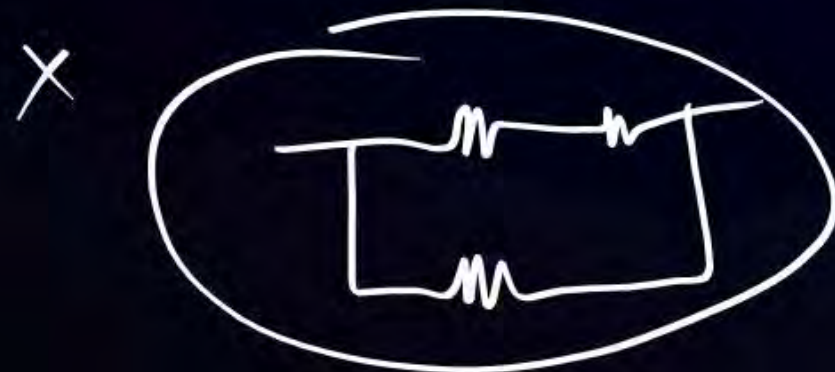
$$= \frac{2}{2} + \frac{2}{2} = 4\ \Omega$$







What is (a) the highest (b) the lowest total resistance that can be secured by combinations of four coils of resistance  $4\ \Omega$ ,  $8\ \Omega$ ,  $12\ \Omega$ ,  $24\ \Omega$ ?

# Note :-


$$a) \quad 4\ \Omega + 8\ \Omega + 12\ \Omega + 24\ \Omega = 48\ \Omega$$

$$b) \quad \frac{1}{R_p} = \frac{1}{4} + \frac{1}{8} + \frac{1}{12} + \frac{1}{24} = \frac{6+3+2+1}{24} = \frac{12}{24}$$

$$R_p = 2\ \Omega$$



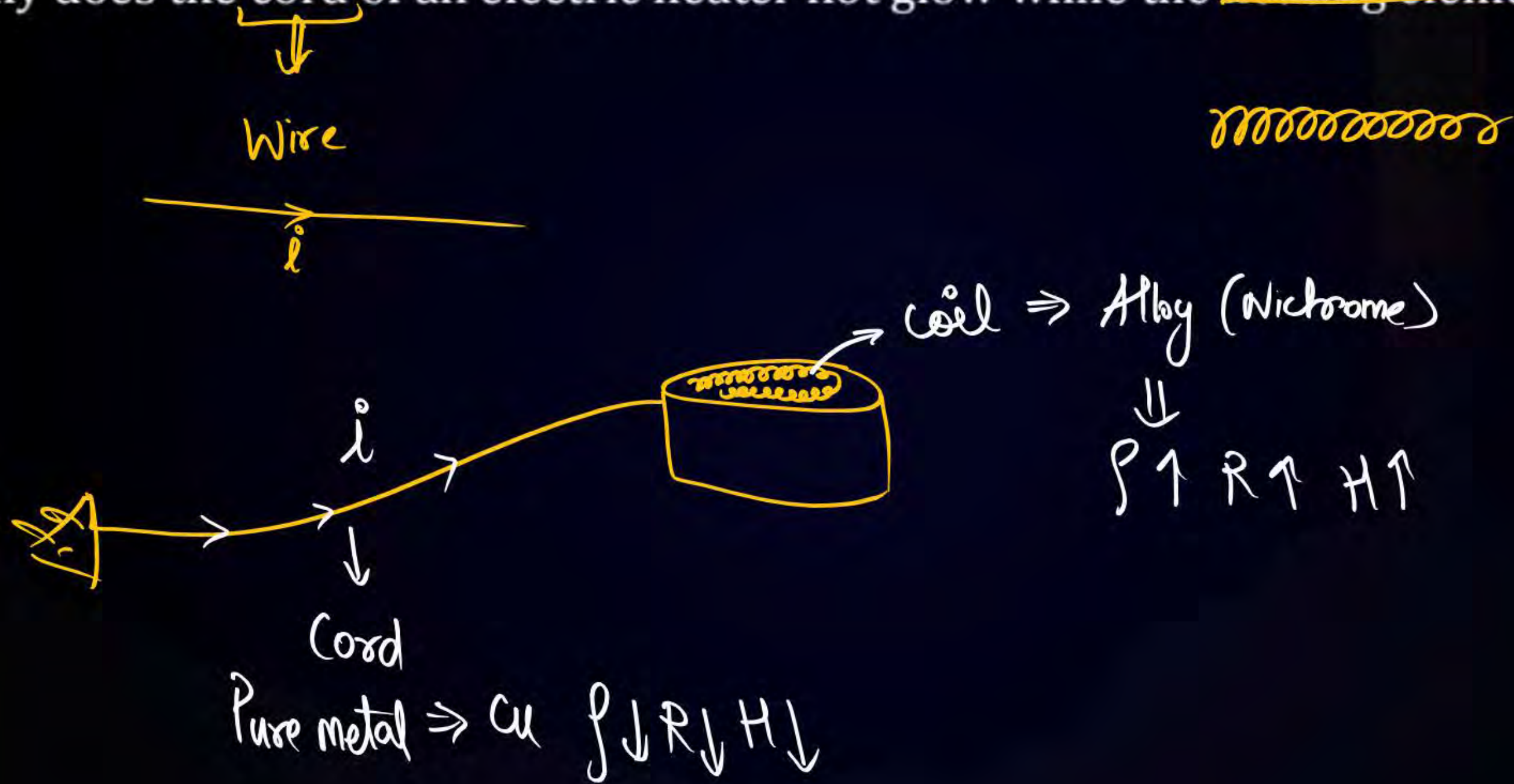Why does the cord of an electric heater not glow while the <sup>Coil</sup> ~~heating element~~ does?



Compute the heat generated while transferring 96000 coulomb of charge in one hour through a potential difference of 50 V.

$$V = 50 \text{ V}$$

$$Q = 96000 \text{ C}$$

$$t = 1 \text{ h}$$

~~$$H = I^2 R t$$~~

~~$$H = \frac{V^2 t}{R}$$~~

~~$$H = V I t$$~~

$$V = \frac{W}{Q}$$

$$W = QV$$

$$= 96000 \times 50$$

$$= \boxed{\phantom{000000}} \text{ J}$$





M.W.

An electric iron of resistance  $20\ \Omega$  takes a current of 5 A. Calculate the heat developed in 30 s.





What determines the rate at which energy is delivered by a current?

Electric Power



An electric motor takes 5 A from a 220 V line. Determine the power of the motor and the energy consumed in 2 h.

$$I = 5 \text{ A}$$

$$V = 220 \text{ V}$$

$$P = ?$$

$$E = ?$$

$$t = 2 \text{ h}$$

$$P = VI$$

$$= 220 \times 5$$

$$P = 1100 \text{ W}$$

$$E = P \times t$$

$$= \frac{1100 \times 2 \text{ h}}{1000}$$

$$= 1.1 \text{ Kw} \times 2 \text{ h}$$

$$E = 2.2 \text{ Kwh} \text{ Ans}$$



H.W. Notes

A piece of wire of resistance  $R$  is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is  $R'$ , then the ratio  $R/R'$  is –

(a)  $1/25$

(b)  $1/5$

(c)  $5$

☒ (d)  $25$



Which of the following terms does not represent electrical power in a circuit?

(a)  $I^2R$

☒ (b)  $IR^2$

(c)  $VI$

(d)  $V^2/R$

$$P = VI$$

$$P = I^2R$$

$$P = \frac{V^2}{R}$$



Imp.

An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be –

(a)  $100 \Omega$

(b)  $75 \Omega$

(c)  $50 \Omega$

☒ (d)  $25 \text{ W}$

$$P = 100 \text{ W}$$

$$V = 220 \text{ V}$$

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{(220)^2}{100} \Omega$$

$$P' = ?$$

$$V = 110 \text{ V}$$

$$R = \frac{(220)^2}{100} \Omega$$

$$P' = \frac{V^2}{R} = \frac{(110)^2}{\frac{(220)^2}{100}} = \frac{110 \times 110 \times 100}{220 \times 220} = 25 \text{ W}$$

$$P = VI \quad \times$$

$$P = \frac{V^2}{R} \quad \checkmark$$

$$P = I^2 R \quad \times$$



H.W.


Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a circuit across the same potential difference. The ratio of heat produced in series and parallel combinations would be –

(a) 1 : 2

(b) 2 : 1

~~(c) 1 : 4~~

(d) 4 : 1

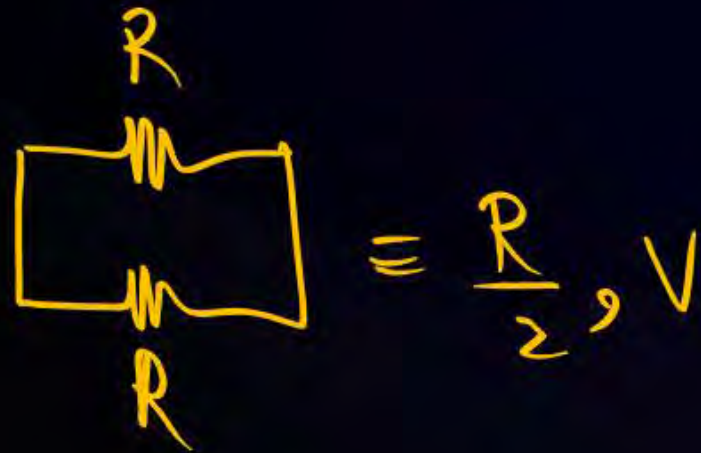

$$H = I^2 R t$$

$$H = \frac{V^2}{R} t$$

$$H = V I t$$


$$\frac{H_s}{H_p} = \frac{\frac{V^2}{2R} \times t}{\frac{V^2}{\frac{R}{2}} \times t} = \frac{1}{2 \times 2} = \frac{1}{4}$$

$H_s : H_p = 1 : 4$



How is a voltmeter connected in the circuit to measure the potential difference between two points?

Parallel

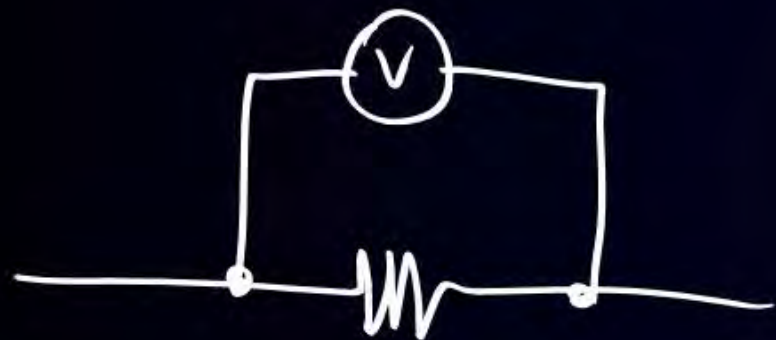

$$d \rightarrow 2d, \quad r \rightarrow 2r, \quad A \rightarrow 4A, \quad R \Rightarrow \frac{R}{4}$$

A copper wire has diameter 0.5 mm and resistivity of  $1.6 \times 10^{-8} \Omega \text{ m}$ . What will be the length of this wire to make its resistance  $10 \Omega$ ? How much does the resistance change if the diameter is doubled?

$$\rightarrow R = 10 \Omega$$

$$d = 0.5 \text{ mm} \times 10^{-3}$$

$$r = \frac{0.5 \times 10^{-3}}{2} \text{ m}$$

$$A = \pi r^2$$

$$\rightarrow A = 3.14 \times \frac{0.5}{2} \times \frac{0.5}{2} \times 10^{-6} \text{ m}^2$$

$$\rightarrow \rho = 1.6 \times 10^{-8} \Omega \text{ m}$$

$$\rightarrow l = ?$$

$$R = \rho \frac{l}{A}$$

$$\frac{RA}{\rho} = l$$

$$l = \frac{RA}{\rho} = \frac{10 \times 3.14 \times \frac{0.5}{2} \times \frac{0.5}{2} \times 10^{-6}}{1.6 \times 10^{-8}}$$

$$= \frac{25}{2} \times \frac{10^{-6}}{10^{-8}}$$


$$= 12.5 \times 10^2 = 1250 \text{ m} \quad \checkmark$$



The values of current  $I$  flowing in a given resistor for the corresponding values of potential difference  $V$  across the resistor are given below –

$I$ (amperes)	0.5	1.0	2.0	3.0	4.0
$V$ (volts)	1.6	3.4	6.7	10.2	13.2

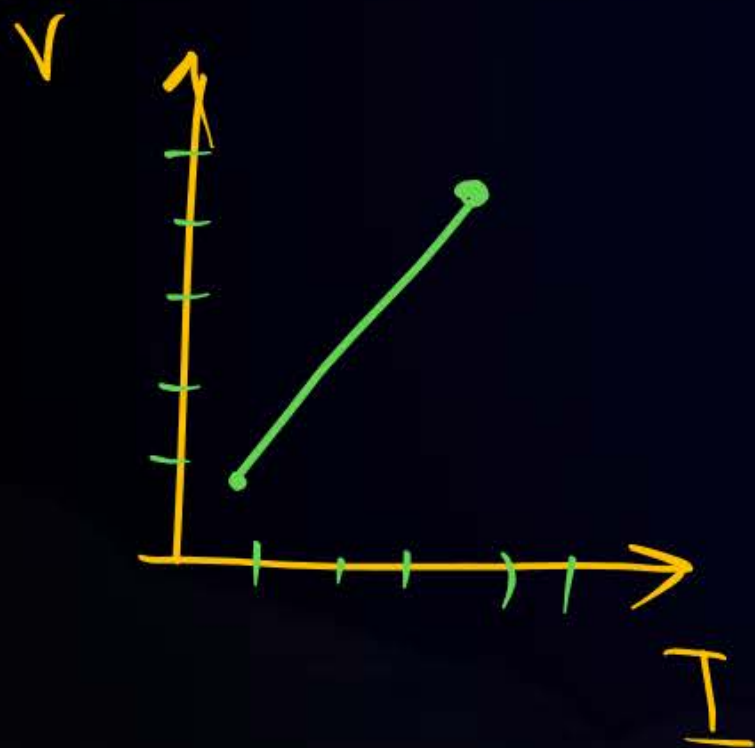Plot a graph between  $V$  and  $I$  and calculate the resistance of that resistor.



$$\begin{aligned} \text{Slope} &= \frac{\Delta y}{\Delta x} = \frac{\Delta V}{\Delta I} = \frac{V_2 - V_1}{I_2 - I_1} = \frac{13.2 - 1.6}{4 - 0.5} \\ &= \left( \right) \Omega \end{aligned}$$

When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.

$$V = 12\text{ V}$$


$$I = 2.5\text{ mA} = 2.5 \times 10^{-3}\text{ A}$$

$$R = ?$$

$$\begin{aligned} R &= \frac{V}{I} = \frac{12}{2.5 \times 10^{-3}} = \frac{12 \times 10^3 \times 10}{25} \\ &= \frac{12 \times 10^4 \times 100}{25} = 4800\ \Omega \end{aligned}$$



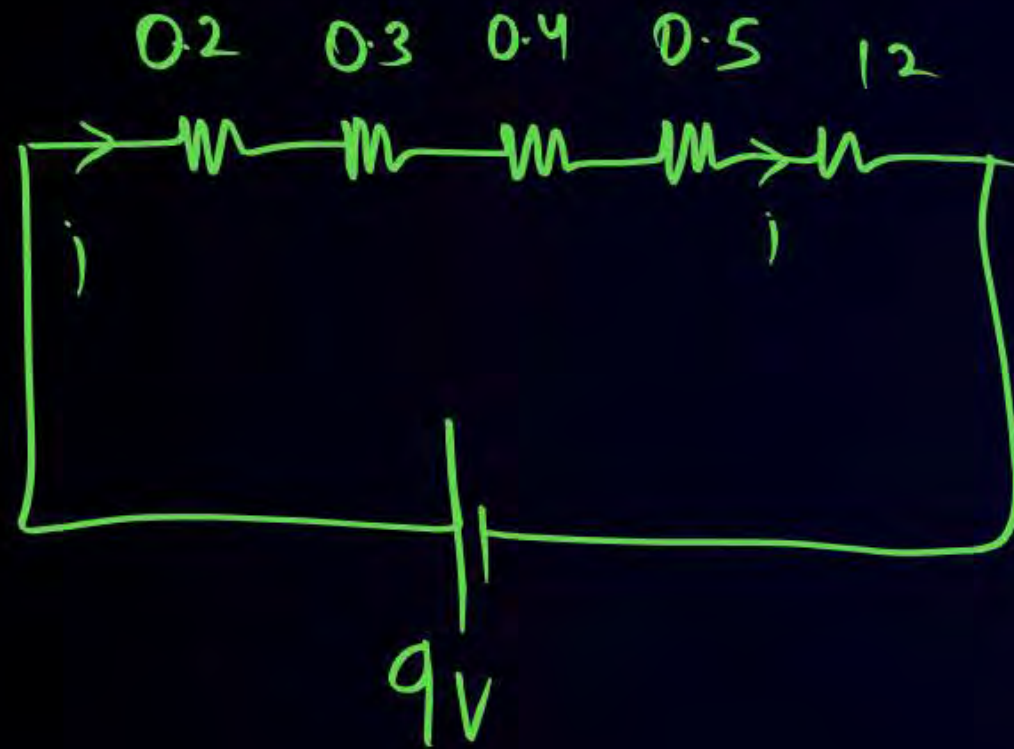A battery of 9 V is connected in series with resistors of  $0.2\ \Omega$ ,  $0.3\ \Omega$ ,  $0.4\ \Omega$ ,  $0.5\ \Omega$  and  $12\ \Omega$ , respectively. How much current would flow through the  $12\ \Omega$  resistor?



$$R_t = 13.4\ \Omega$$

$$V = 9\text{ V}$$


$$i = \frac{V}{R} = \frac{9}{13.4}\text{ A}$$

How many 176  $\Omega$  resistors (in parallel) are required to carry 5 A on a 220 V line?

$$V = 220 \text{ V}$$

$$I = 5 \text{ A}$$
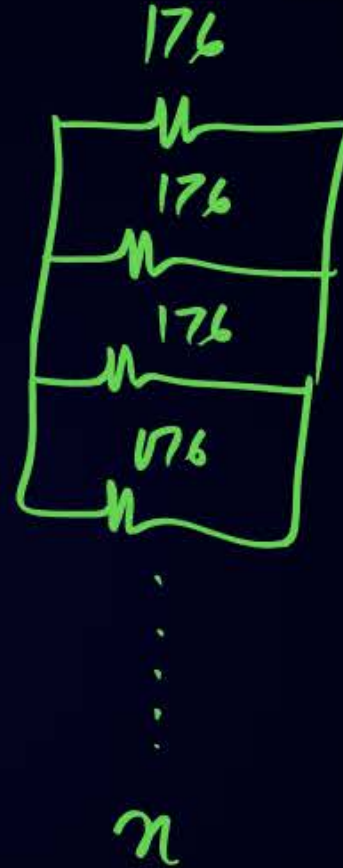
$$R_t = \frac{V}{I} = \frac{220}{5} = 44 \Omega$$



$$\frac{1}{R_t} = \frac{1}{176} + \frac{1}{176} + \frac{1}{176} \dots n$$

$$\frac{1}{44} = \frac{n}{176}$$

$$n = \frac{176}{44}$$

$$n = 4 \text{ Ans}$$





H.W.



Show how you would connect three resistors, each of resistance  $6\ \Omega$ , so that the combination has a resistance of (i)  $9\ \Omega$ , (ii)  $4\ \Omega$ .

Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel with each other across the two wires of 220 V line if the maximum allowable current is 5 A?


$$V = 220 \text{ V}$$

$$i = 5 \text{ A}$$

$$P_t = Vi$$

$$= 220 \times 5$$

$$= 1100 \text{ W}$$

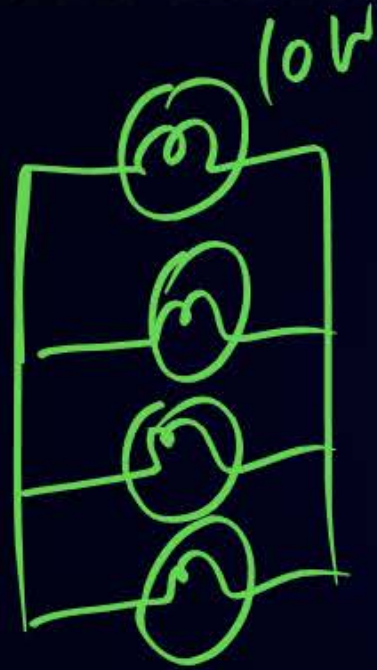

$$P_t = P + P + P + \dots + n$$

$$1100 = 10 + 10 + 10 + \dots + n$$

$$1100 = 10n$$

$$n = 110 \text{ bulbs}$$



A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of  $24\ \Omega$  resistance, which may be used separately, in series, or in parallel. What are the currents in the three cases?

Case I




$$I = \frac{V}{R} = \frac{220}{24} \text{ A}$$

Case II



$$I = \frac{220}{48} \text{ A}$$


Case III

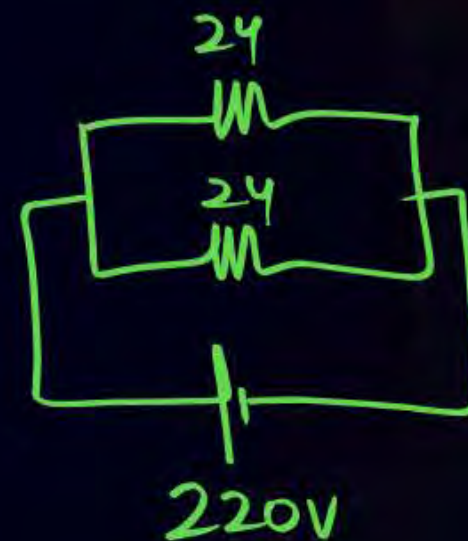

$$I = \frac{V}{R} = \frac{220}{12} \text{ A}$$



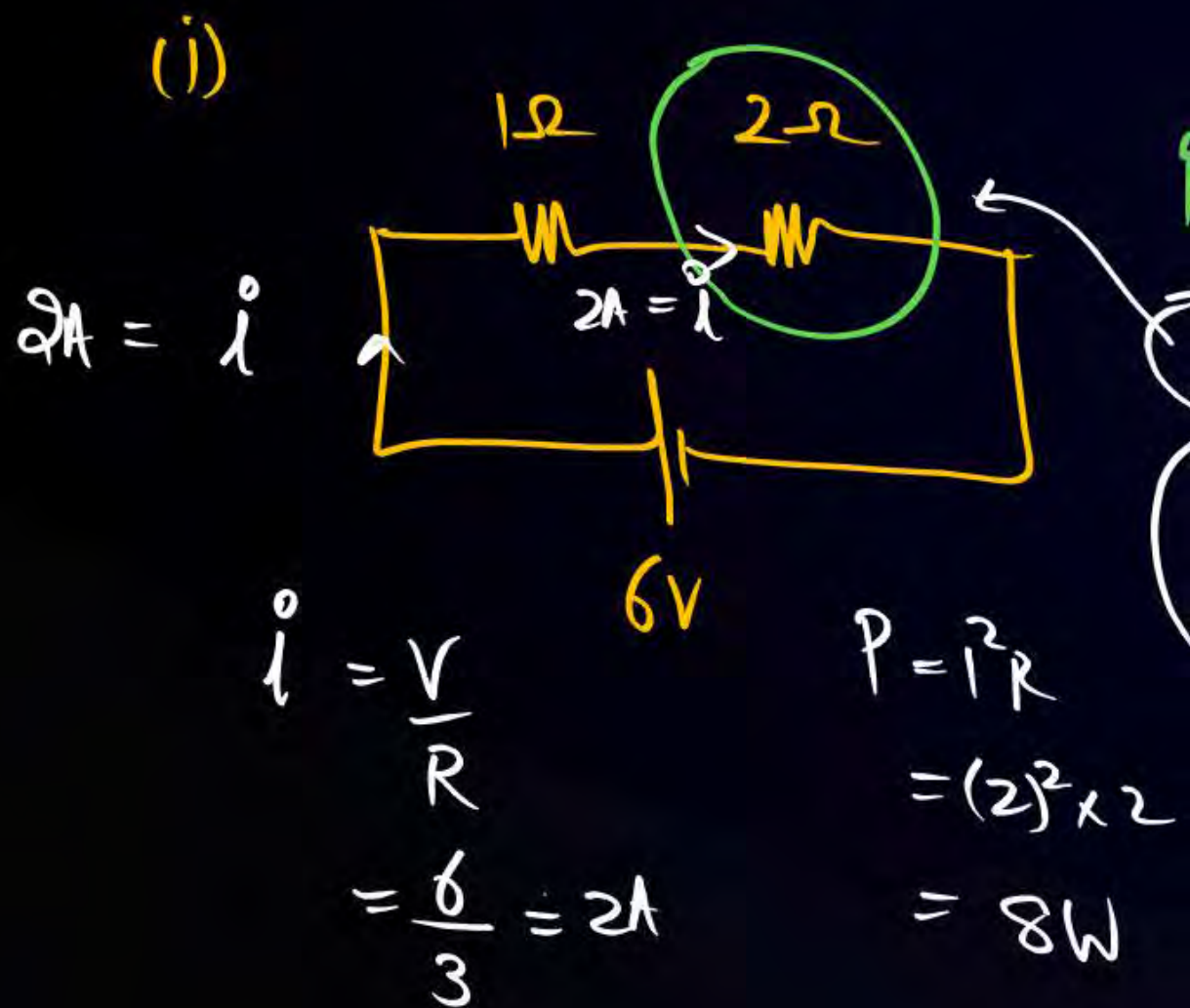Compare the power used in the  $2\ \Omega$  resistor in each of the following circuits: (i) a 6 V battery in series with  $1\ \Omega$  and  $2\ \Omega$  resistors, and (ii) a 4 V battery in parallel with  $12\ \Omega$  and  $2\ \Omega$  resistors.




(ii)

$P = VI$

$P = I^2 R$

$P = \frac{V^2}{R}$

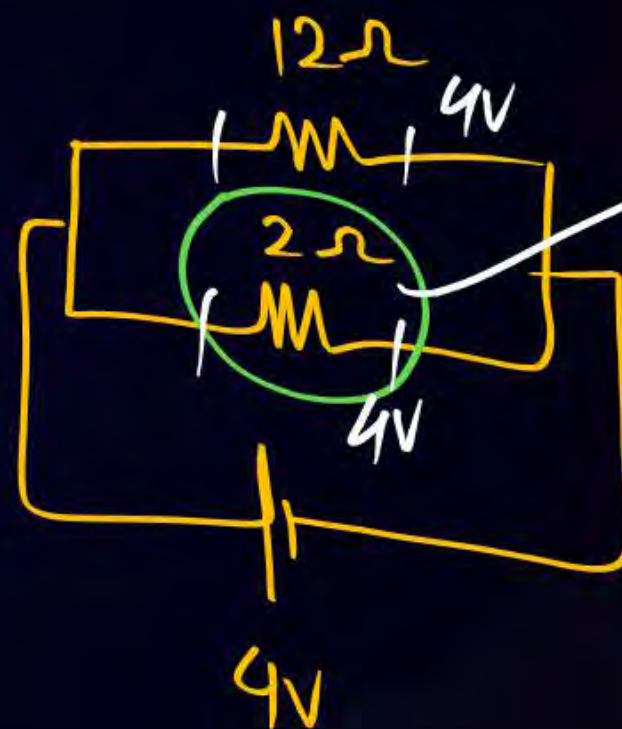


$P = \frac{V^2}{R}$

$= \frac{(4)^2}{2} = \frac{16}{2}$

$= 8W$



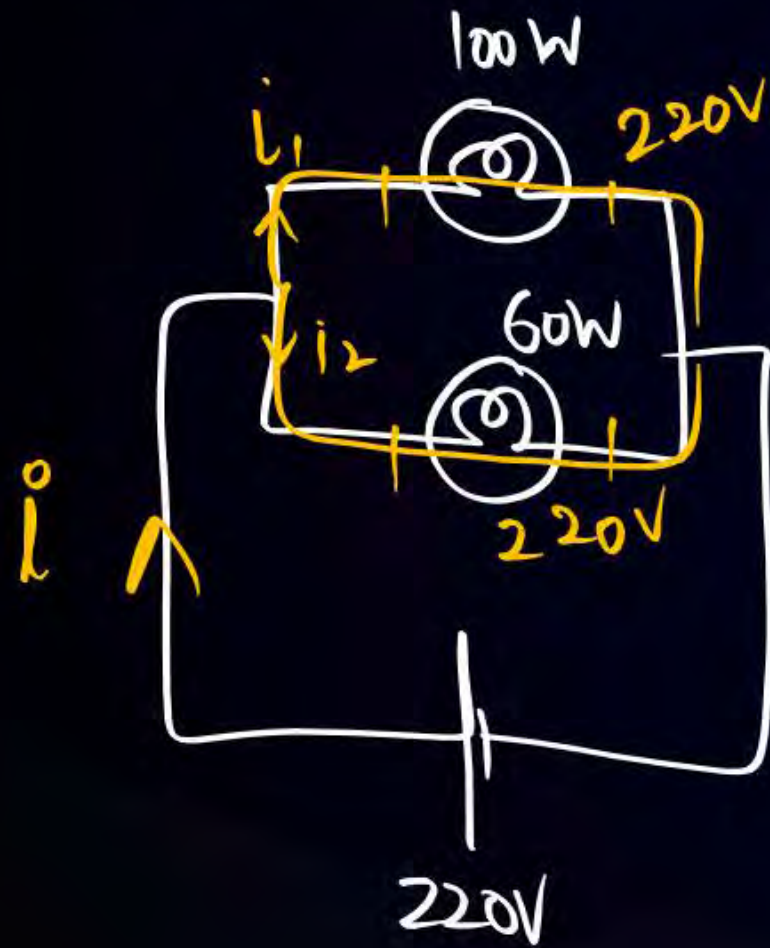Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V?



$$P = Vi_1$$
$$100 = 220 \times i_1 \rightarrow i_1 = \frac{100}{220} \text{ A}$$

$$P = Vi_2$$
$$60 = 220 \times i_2 \rightarrow i_2 = \frac{60}{220} \text{ A}$$

$$i = i_1 + i_2$$

$$= \frac{100}{220} + \frac{60}{220}$$

$$i_t = \frac{8+60}{220} = \frac{8}{11} \text{ A}$$

$$i_t = \frac{8}{11} \text{ A}$$

Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes?

TV

$$P = 250 \text{ W}$$

$$t = 1 \text{ h}$$

$$E = P \times t$$

$$= \frac{250}{1000} \times 1$$

$$= 0.25 \text{ KWh}$$

Toaster

$$P = 1200 \text{ W}$$

$$t = \frac{10 \text{ min}}{60} = \frac{10}{60} \text{ h}$$

$$E = P \times t$$

$$= \frac{1200}{1000} \times \frac{10}{60}$$

$$= 0.2 \text{ KWh}$$



An electric heater of resistance  $8\ \Omega$  draws  $15\text{ A}$  from the service mains  $2\text{ hours}$ .  
Calculate the rate at which heat is developed in the heater.

✓  $R = 8\ \Omega$

✓  $i = 15\text{ A}$

✓  $t = 2\text{ h}$

$$P = i^2 R$$

$$= (15)^2 \times 8$$

$$= 225 \times 8\text{ Watt}$$

Explain the following.

- (a) Why is the tungsten used almost exclusively for filament of electric lamps?
- (b) Why are the conductors of electric heating devices, such as bread-toasters and electric irons, made of an alloy rather than a pure metal?
- (c) Why is the series arrangement not used for domestic circuits?
- (d) How does the resistance of a wire vary with its area of cross-section?
- (e) Why are copper and aluminium wires usually employed for electricity transmission?

$$R \propto \frac{1}{A}$$

↓  
light weight



**Thank**  
*You*

