

UPDAAN

2025

ELECTRICITY

PHYSICS

Lecture – 03

By – ER. RAKSHAK SIR



Topics to be covered



- 1 OHM'S LAW ✓
- 2 RESISTANCE ✓
- 3 VERIFICATION OF OHM'S LAW ✓
- 4 FACTORS AFFECTING RESISTANCE
- 5 DIFFERENCE BETWEEN
- 6 RESISTIVITY OF ELECTRICAL SUBSTANCES



* Pichli Kakshao Ka Nichod

$$10A \rightarrow \frac{10C}{1s}$$

① Charge (Q)

→ SI unit → Coulomb (C)

Attraction / Repulsion

→ Quantization

$$1e^- = 1.6 \times 10^{-19} C$$

$$Q = ne$$

Net charge no. of electrons

② Current = $\frac{\text{charge}}{\text{time}}$

$$I = \frac{Q}{t}$$

$$A = \frac{C}{s}$$

3C / 1s → $3A = \frac{3C}{1s}$

2C / 1s → $2A = \frac{2C}{1s}$

③ Voltage = $\frac{\text{Workdone}}{\text{Charge}}$
(Pot. diff.)



$$V = 0, I = 0$$

$$V = 2V = \frac{2J}{1C}$$

$$V = 100V = \frac{100J}{1C}$$



ELECTRICAL CIRCUIT



Que. What is an Electric Circuit ?

Ans. A continuous and closed path made up of wires on which an electric current runs is called an electric circuit. An electric circuit consists of electric devices, a source of energy and wires that are connected with the help of a switch.

- $\text{---} \text{ⓐ} \text{---}$ 1) Ammeter
 $\text{---} \text{Ⓥ} \text{---}$ 2) Voltmeter
 $\text{---} \text{|||||} \text{---}$ 3) Battery

- 4) Rheostat $\text{---} \text{⏏} \text{---}$
5) Key $\text{---} () \text{---}$
6) Resistance $\text{---} \text{⏏} \text{---}$

Plug in \rightarrow ON
Plug out \rightarrow OFF

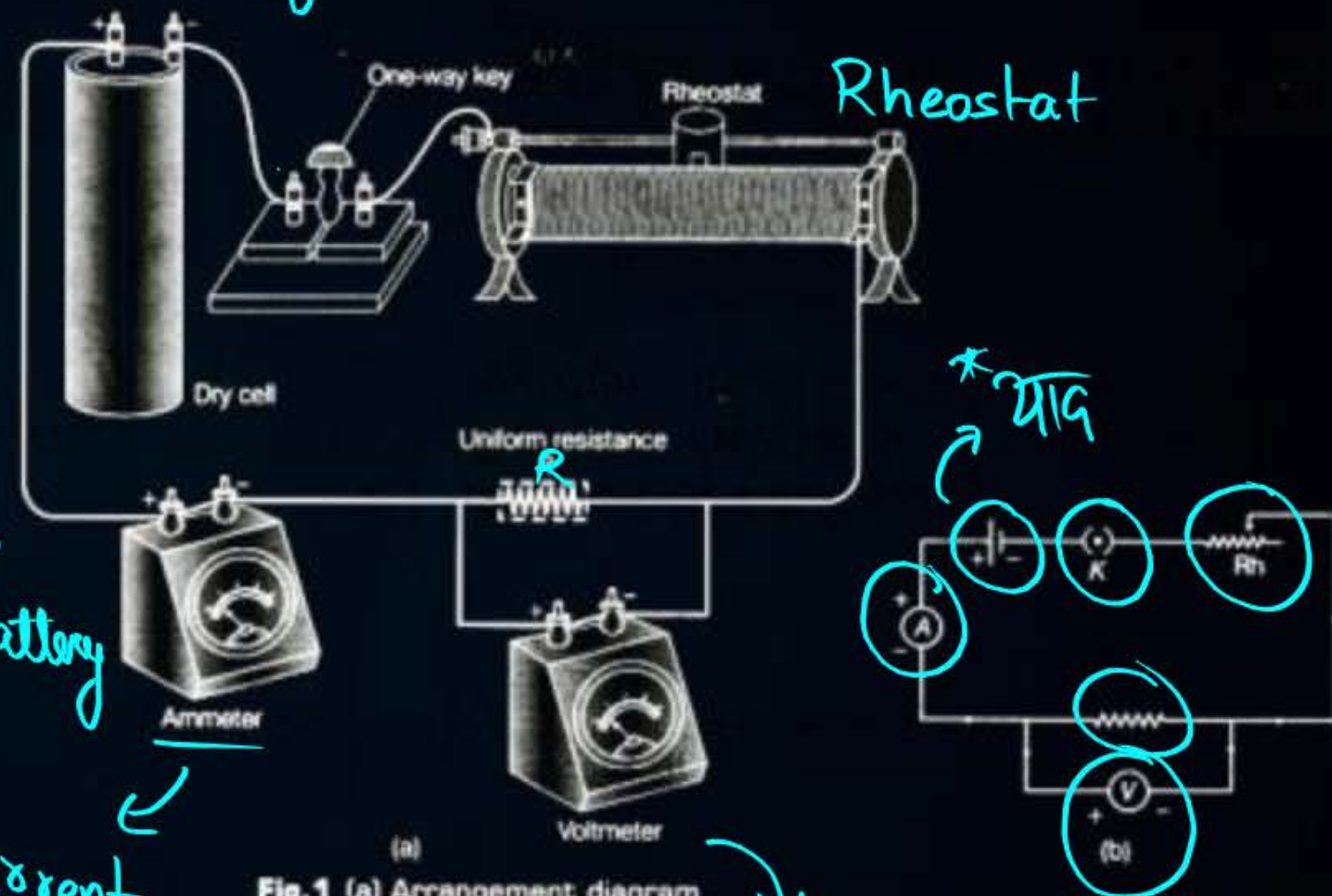


Fig. 1 (a) Arrangement diagram
(b) Circuit diagram



CIRCUIT ELEMENTS



S. No.	Components	Symbols
★ 1 ✓	An electric cell	
✓ 2	A <u>battery</u> or a combination of cells	
✓ 3	Plug key or switch (<u>open</u>) Plug out	$I = 0$ 'OFF'
★ 4 ✓	Plug key or <u>switch</u> (<u>closed</u>) Plug in	$I \neq 0$ 'ON'
✓ 5	A wire joint	
✓ 6	Wires crossing without joining	
✓ 7	Electric bulb	
★ 8 ✓	A resistor of resistance R	
★ 9 ✓	Variable resistance or rheostat	
★ 10	Ammeter	
★ 11	Voltmeter	



cell



Combination of cells
or
Battery





CIRCUIT ELEMENTS



Voltage



BATTERY
ELIMINATORS



RESISTANCE
BOX



VOLTMETER



AMMETER



PLUG KEY



RHEOSTAT (Baad Mein)




CONNECTING
WIRE



AMMETER, VOLTMETER



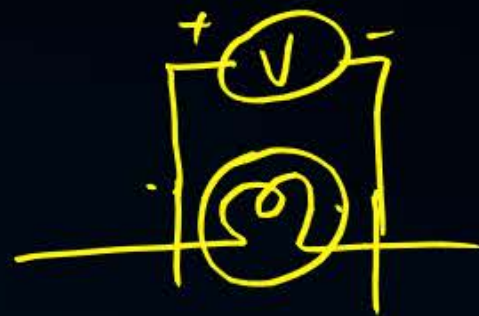- Current measuring device
- Always connect in series with the device
- Ideal Ammeter ($R \approx 0$)



- Voltage measuring device
- Always connected across parallel with the device
- Ideal Voltmeter ($R \approx \infty$)




OHM'S LAW

$$V=0$$
$$I=0$$



Voltage ↓ Current ↓

Voltage ↑ Current ↑

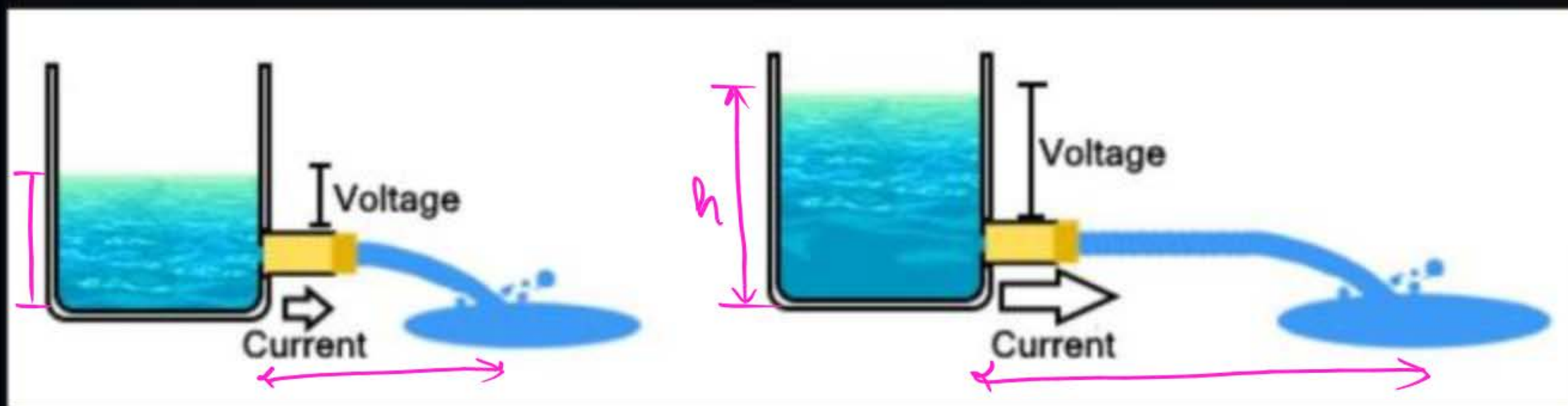

I
flow less level low

II
flow high level high

①

Ohm's law states that, " Current flowing in a conductor is directly proportional to the amount of potential difference applied across the ends of the conductor, at a constant temperature".

Voltage \propto Current

$$V \propto I$$


$$V = IR$$

Diagram illustrating Ohm's Law: A rectangular box contains the equation $V = IR$. Arrows point from the terms to their definitions: V points to "Voltage", I points to "Current", and R points to "Resistance". A small star symbol is at the top left corner of the box.

RESISTANCE


→ 'Rukawat'

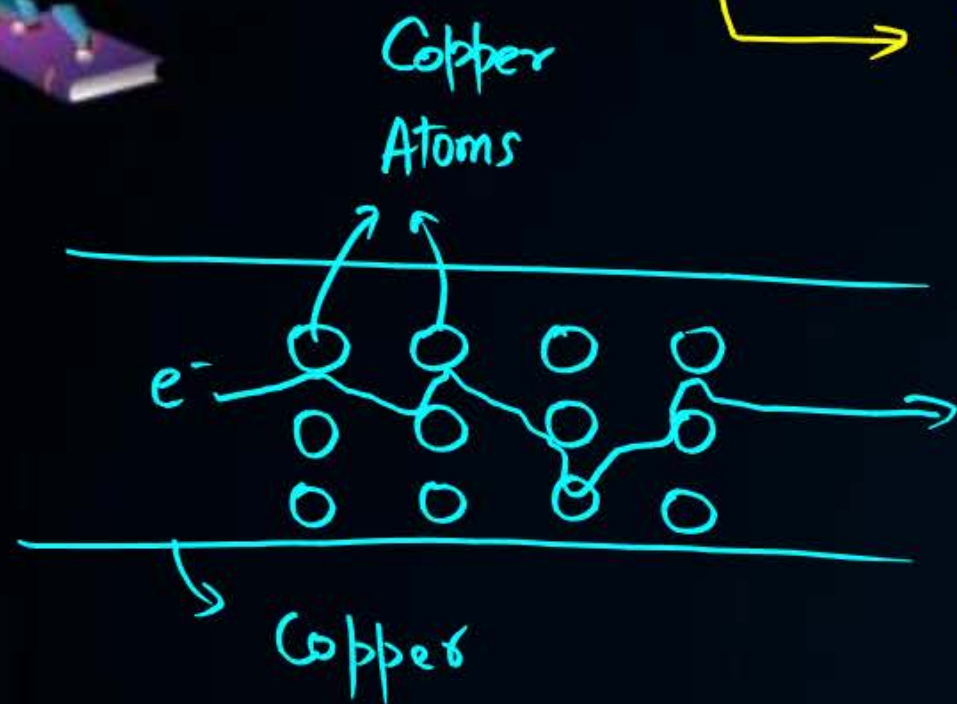Define - The opposition offered by the atoms of the conductor in the path of moving electron.



Denote → 'R'

SI Unit → 'Ohm' (Ω)

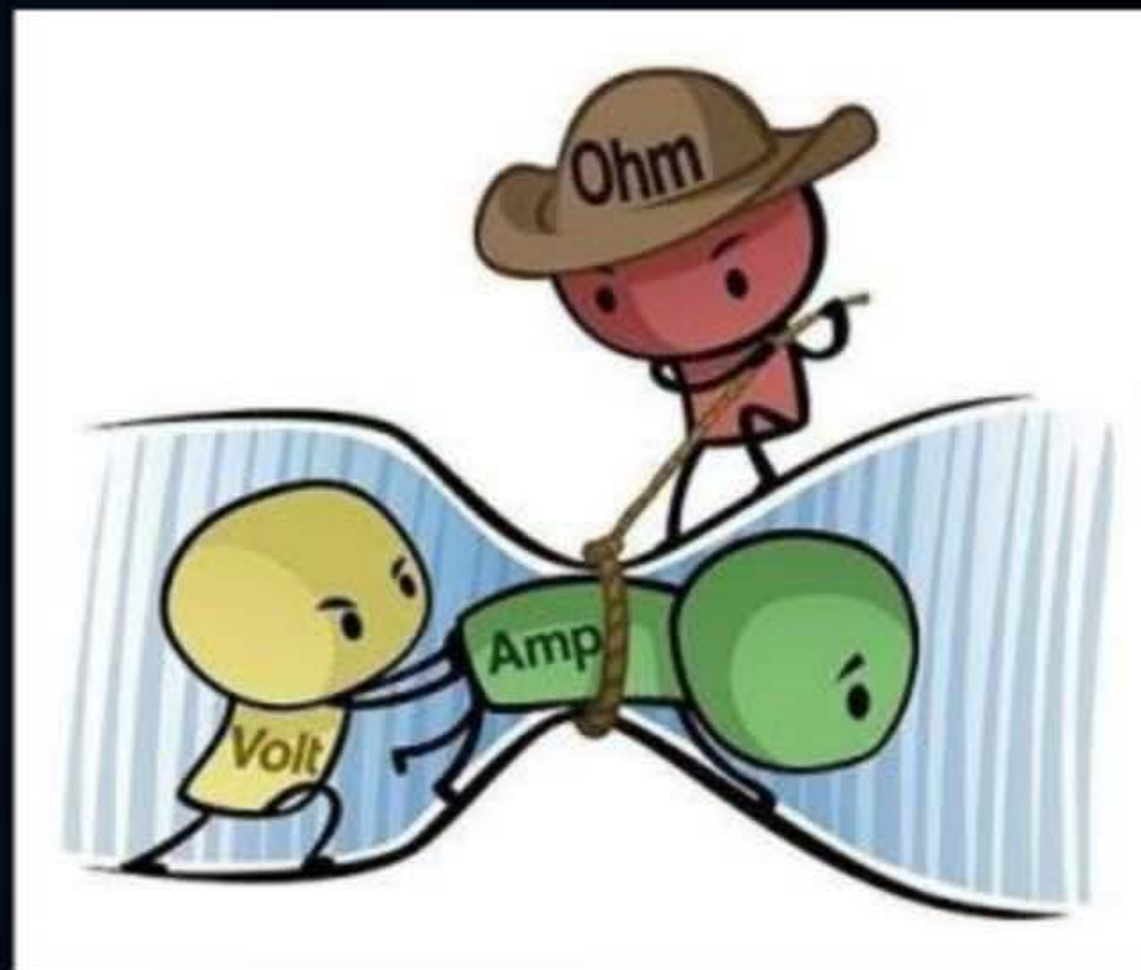

QUESTION



How much current will an electric bulb draw from a 220 V source, if the resistance of the bulb filament is 1200 Ω ?

$$V = 220 \text{ V}$$

$$R = 1200 \Omega$$

$$I = ?$$

$$V = IR$$

$$220 = I \times 1200$$

$$I = \frac{220}{1200}$$

$$I = \frac{11}{60} \text{ A}$$



THANK
YOU

